

Qucs

A Tutorial Getting Started with Digital Circuit Simulation

Mike Brinson

Copyright © 2006 Mike Brinson <mbrin72043@yahoo.co.uk>

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.1 or any later version published by the Free Software Foundation. A copy of the license is included in the section entitled "GNU Free Documentation License".

Introduction

On 21 January 2006 Qucs 0.0.8 was released by the Qucs development team. This is the first version of the package to include digital circuit simulation based on VHDL. FreeHDL¹ being chosen as the VHDL engine. In the period following the release of Qucs 0.0.8 there has been considerable activity centred around finding and correcting a number of bugs in the Qucs digital simulation code. Many of these fixes are now included in the latest CVS code and will eventually form part of the next Qucs release. This tutorial note is an attempt on my part to communicate to other Qucs users a number of background ideas concerning the capabilities and limitations of the current state of Qucs VHDL simulation. Much of the information reported here was assembled by the author while assisting Michael Margraf to test and debug the VHDL code generated by Qucs. In the future, if there is enough interest in these notes, or indeed in Qucs VHDL simulation in general, I will update them as the Qucs digital simulation features are improved.

Qucs digital simulation follows a complex set of steps that are mostly transparent to the software user. In step one, a schematic representing a digital circuit under test is drawn. This schematic consists of an interconnected group of Qucs digital components, one or more user defined digital subcircuits (if required), and a copy of the digital simulation icon with the timing or truth table parameters set. In step two, the information recorded on a circuit schematic is converted into a text file containing VHDL statements. These describe the circuit components, their connection, and a testbench for simulating circuit performance. Next, FreeHDL is launched by Qucs to convert the VHDL code file into a C++ source program. This is compiled to form an executable machine code simulation of the original circuit. Finally, Qucs runs this program, collects signal data as digital signal events take place and displays signal waveforms as a function of time or digital data in a truth table format.

The VHDL code generated by Qucs 0.0.8 is limited in its scope by the following factors:

- Digital gates are described by data flow concurrent statements.
- Flip-flops and the digital signal generator are described by process statements.
- Component connection wires (signals) can only be of type bit as defined in the standard VHDL library².

¹The FreeHDL Project, <http://www.freehdl.seul.org/>.

²Signal type bit only defines logic signals '0' and '1'. Care must be taken to ensure that signal

- Digital bus structures are not allowed in this release of the Qucs package.
- Digital subcircuits can be drawn as schematics and associated with a symbol in a similar fashion to analogue subcircuits.
- Digital subcircuit pins can have type in, out, inout or analog. Qucs treats pins of type analog the same as VHDL pin type inout.
- Once defined digital subcircuits may be placed and connected to other components on schematics.
- Multiple copies of the same digital subcircuit are allowed on a single schematic.
- Digital subcircuits may also be nested; nesting has been tested to a depth of four.

Simulating simple digital circuits

The most basic form of digital circuit that can be simulated is one consisting entirely of Qucs predefined digital components drawn on a schematic having only one level of design hierarchy. The truth table for a simple combinational circuit of this type is shown in Table 1.

Output F can be expressed in sum of products Boolean form as

$$F = \overline{A}.\overline{B}.C + \overline{A}.B.\overline{C} + A.\overline{B}.C + A.B.\overline{C}$$

contention does not occur during simulation because the resulting logic state cannot be modelled with type bit. Signal contention can happen when two or more digital devices attempt to drive the same wire with logic '0' and logic '1' signals at the same time. Moreover, it is not possible to simulate the performance of tristate devices using VHDL signal type bit.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Table 1: Truth table for a logic circuit with inputs A, B, C and output F.

On minimisation, using Boolean algebra or a Karnaugh map, output F becomes

$$F = A.C + B.\overline{C}$$

The schematic for example 1 is illustrated in Fig. 1. This diagram was constructed using the same techniques employed for drawing analogue schematics.

Notes on drawing digital schematics

- The only predefined Qucs components that can be used to draw a digital circuit schematic are (1) the digital components listed in the digital components icon window, (2) the ground symbol, and (3) the digital simulation icon.
- A useful tip when drawing digital schematics is to adopt the matrix approach shown in Fig. 1. Input signals flow from top to bottom of the schematic and output signals are positioned on the right-hand side of a horizontal line. This makes checking the circuit schematic for errors much easier than the case where diagrams have wires connecting components in an unstructured way.
- Input and output wires (signals) should be given names consistent with the circuit being simulated, A, B, C and F in Fig. 1. If the signal wires are not named by the user, Qucs will allocate them different arbitrary names. This can make identification and selection of signals for display on an output waveform graph, and indeed checking for errors in a large circuit, much more difficult than it need be.
- Notice in Fig. 1 the international symbols for the logic gates are shown on the schematic.

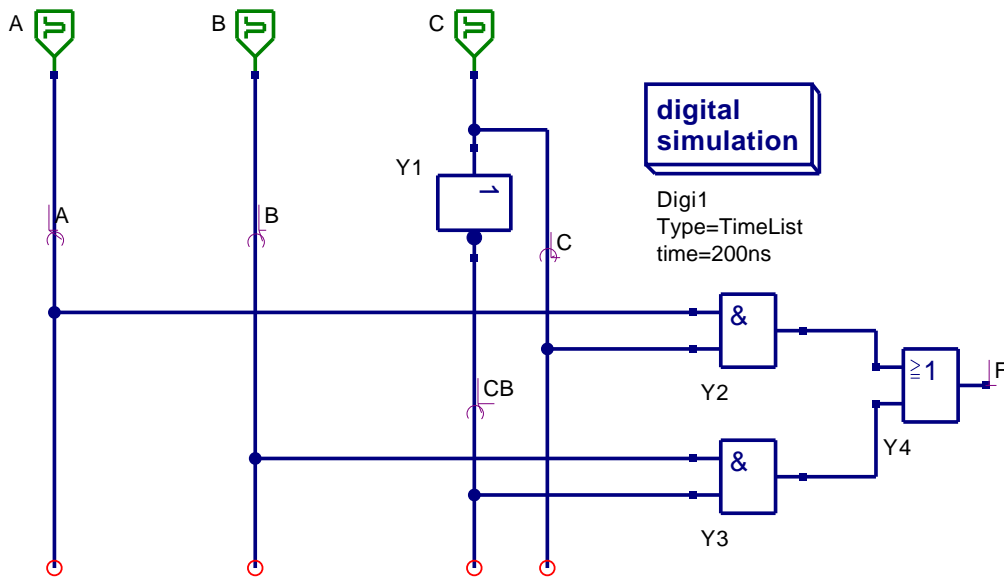


Figure 1: Qucs schematic for minimised logic function F.

VHDL code generated by Qucs

Clicking the Qucs Simulate menu button (or pressing key F2) starts the simulation process. At an early phase in this process Qucs writes a text file to disk that contains the VHDL code for the circuit being simulated. This file can be displayed by clicking on the *show last netlist* drop down menu or by pressing key F6. The VHDL code produced by Qucs for the circuit shown in Fig. 1 is presented in Table 2.

Signals identified by nnnet0 and nnnet1 in Table 2 have been allocated these names by Qucs; nnnet0 and nnnet1 are internal signal nets that are not named on the circuit schematic shown in Fig. 1. Fig. 2 illustrates the starting section of a typical Qucs digital functional waveform plot. This style of plot illustrates signal events without component delays. If required, signal delays can be specified for individual gates and other components (from the component *edit properties* menu). The VHDL code generated for components with delays will then reflect such changes, for example adding a 10 ns delay to signal CB in Table 2 generates VHDL code

```
CB <= not C after 10 ns;
```

Readers will probably have observed that the Qucs version number referred to in Table 2 VHDL listing is 0.0.9. This is the current CVS development version number. Qucs 0.0.9 includes a number of important bug fixes. The remainder of these notes assume readers have downloaded, and recompiled, the latest CVS code

```

— Qucs 0.0.9  tut1_ex1.sch
entity TestBench is
end entity;
use work.all;

architecture Arch_TestBench of TestBench is
signal CB, A, B, F, C,
        nnnet0,
        nnnet1 : bit;
begin
    nnnet0 <= C and A;
    nnnet1 <= CB and B;
    CB <= not C;

    A:process
    begin
        A <= '0'; wait for 40 ns;
        A <= '1'; wait for 40 ns;
    end process;

    B:process
    begin
        B <= '0'; wait for 20 ns;
        B <= '1'; wait for 20 ns;
    end process;

    F <= nnnet1 or nnnet0;

    C:process
    begin
        C <= '0'; wait for 10 ns;
        C <= '1'; wait for 10 ns;
    end process;

end architecture;

```

Table 2: VHDL code for the circuit shown in Fig. 1.

from Sourceforge.net³.

 


Figure 2: Digital functional waveforms for the circuit shown in Fig. 1.

Truth tables

Truth tables are one of the most fundamental and convenient ways of displaying digital circuit data. Qucs has a built-in facility that allows a truth table to be generated from a schematic drawing. This feature is particularly useful when checking minimised logic designs for errors. Lets consider a simple but instructive example: A logic circuit has four binary inputs A, B, C, and D, and one output P. Output P is logic '1' when inputs ABCD are numbers in the decimal sequence 3, 5, 7, 11 and 13. In Boolean sum of product form

$$P = \overline{A}.\overline{B}.C.D + \overline{A}.B.\overline{C}.D + \overline{A}.B.C.D + A.\overline{B}.C.D + A.B.\overline{C}.D$$


This simplifies to

$$P = D.(A.B + B \oplus C)$$


The schematic for the sum of products equation for P is shown in Fig. 3(a). Similarly Fig. 3(b) presents the schematic for a minimised P equation. Setting the digital simulation type to TruthTable, rather than TimeList, causes Qucs on pressing key F2, to generate a truth table based on the information provided on a circuit schematic. The number of truth table inputs, and indeed outputs, correspond to the number of input generators and the number of named outputs. Truth tables for both schematics are given in Table 3(a) and 3(b). Comparing these two tables clearly indicates that they are not identical and moreover confirms that the minimised solution is not correct. Reworking the minimisation procedure points to the error being a missing signal inversion. The correct Boolean equation for P is

$$P = D.(\overline{A}.B + B \oplus C)$$

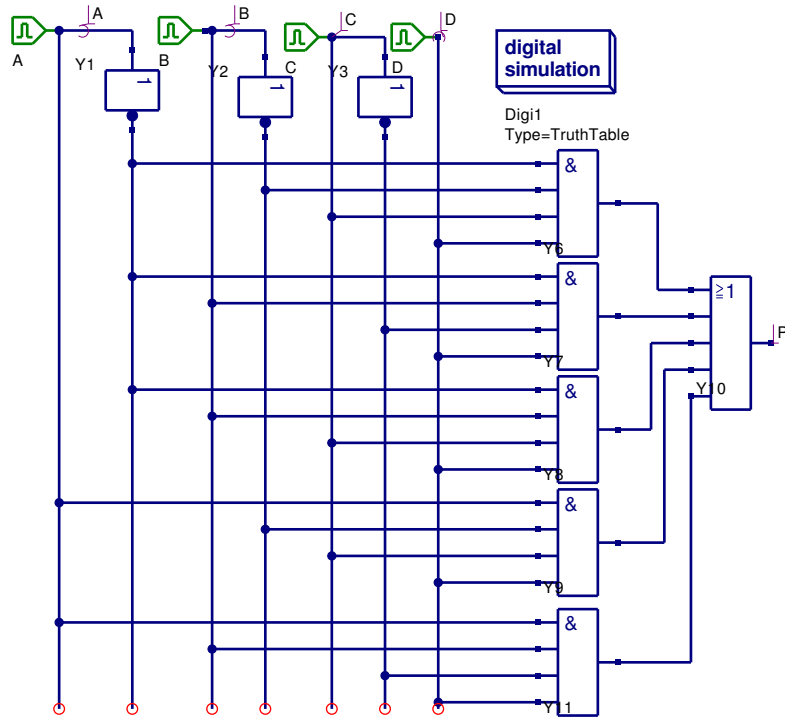³Please note, Qucs Linux release 0.0.8 will normally simulate single hierarchy digital circuits without error. However, Qucs 0.0.8 does fail at the VHDL to C++ conversion phase if a schematic includes more than one ground symbol.



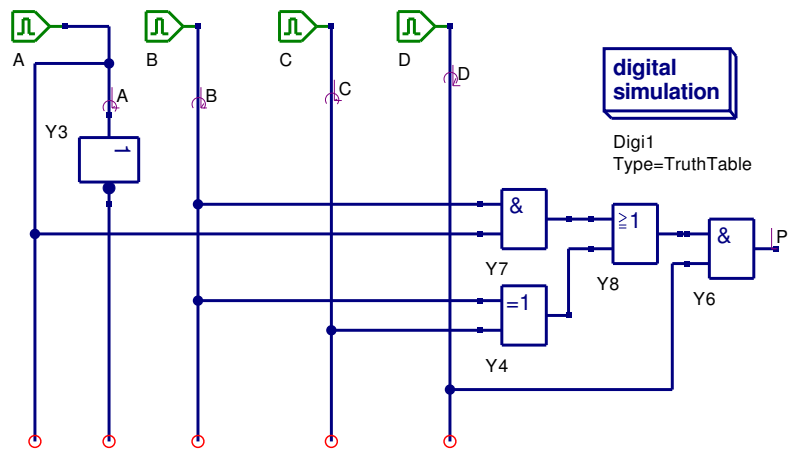3(a): Schematic diagram for sum of products equation P



3(b): Schematic diagram for minimised equation P

3(a): Truth table for sum of products equation P

▲		a.X	b.X	c.X	d.X	p.X
	00000	0	0	0	0	0
	00001	0	0	0	1	0
	00010	0	0	1	0	0
	00011	0	0	1	1	1
	00100	0	1	0	0	0
	00101	0	1	0	1	1
	00110	0	1	1	0	0
	00111	0	1	1	1	1
	01000	1	0	0	0	0
	01001	1	0	0	1	0
	01010	1	0	1	0	0
	01011	1	0	1	1	1
	01100	1	1	0	0	0
	01101	1	1	0	1	1
	01110	1	1	1	0	0
▼	01111	1	1	1	1	0

3(b): Truth table for minimised equation P

▲		a.X	b.X	c.X	d.X	p.X
	00000	0	0	0	0	0
	00001	0	0	0	1	0
	00010	0	0	1	0	0
	00011	0	0	1	1	1
	00100	0	1	0	0	0
	00101	0	1	0	1	1
	00110	0	1	1	0	0
	00111	0	1	1	1	0
	01000	1	0	0	0	0
	01001	1	0	0	1	0
	01010	1	0	1	0	0
	01011	1	0	1	1	1
	01100	1	1	0	0	0
	01101	1	1	0	1	1
	01110	1	1	1	0	0
▼	01111	1	1	1	1	1

Digital subcircuits

Although it is possible to draw complex schematic diagrams using only the pre-defined digital components supplied with Qucs, this technique can be extremely tedious, and is of course, prone to error. When drawing large schematics we require a design procedure that naturally subdivides groups of digital components into self contained units. These units can then be treated in the same way as basic digital components when placing and connecting them on a schematic drawing. In the world of analogue and digital circuit design such units are often called subcircuits.⁴ A subcircuit is defined by three major attributes plus a number of other properties. The major attributes are, firstly a digital circuit that defines circuit function, secondly a circuit symbol that depicts a circuit in a higher level of a design hierarchy, and thirdly the subcircuit input/output pins shown on the subcircuit symbol. Other properties include for example, signal path delays. The process for generating digital subcircuits is identical to that used for analogue subcircuits. It is best demonstrated by considering an example. Figure 4 shows the schematic for a four input combinational circuit.

After drawing a subcircuit schematic, input and output⁵ pins are attached to signal ports. Input port pins of type in are shown on circuit diagrams as a green symbol, signals W, X, Y, and Z, in Fig. 4. Output port pins of type out are coloured red, signal G in Fig. 4. Signal flow through a port is indicated by the direction of the port symbol arrow head. Input/output signals, and any other signals that need to be easily identified, are also named. Once the subcircuit schematic is complete, pressing key F3 causes Qucs to generate a subcircuit symbol. The drawing tools listed as icons in the Qucs paintings window can be used to edit Qucs generated subcircuit symbols. The input/output port pins on a subcircuit symbol have the same type and name as those on the original subcircuit schematic. Fig. 5 shows the finished symbol for subcircuit COMB1. In these notes, symbol outlines are shown drawn in accordance with the international code for logic symbols⁶. To test our new subcircuit we place it's symbol on a blank drawing sheet and apply test signals to the input pins and observe the signals at the output pin. Fig. 6 shows a typical test circuit. Subcircuit Gen4bit generates a 4 bit test pattern synchronised

⁴The circuit simulator SPICE is a well known example of a widely used CAD program that makes extensive use of subcircuits in circuit design.

⁵Qucs 0.0.8 has a bug which causes a VHDL compile error when subcircuit pins are specified as type out. A work around for this bug is to specify subcircuit output pins as type analog. The Qucs routines that generate the circuit VHDL code convert pin type analog into VHDL type inout. FreeHDL is then able to compile the generated VHDL code without error. This bug has been corrected in Qucs 0.0.9.

⁶Ian, Kampel, A practical introduction to the new logic symbols, Butterworths, 1985, ISBN 0-408-01461-X.

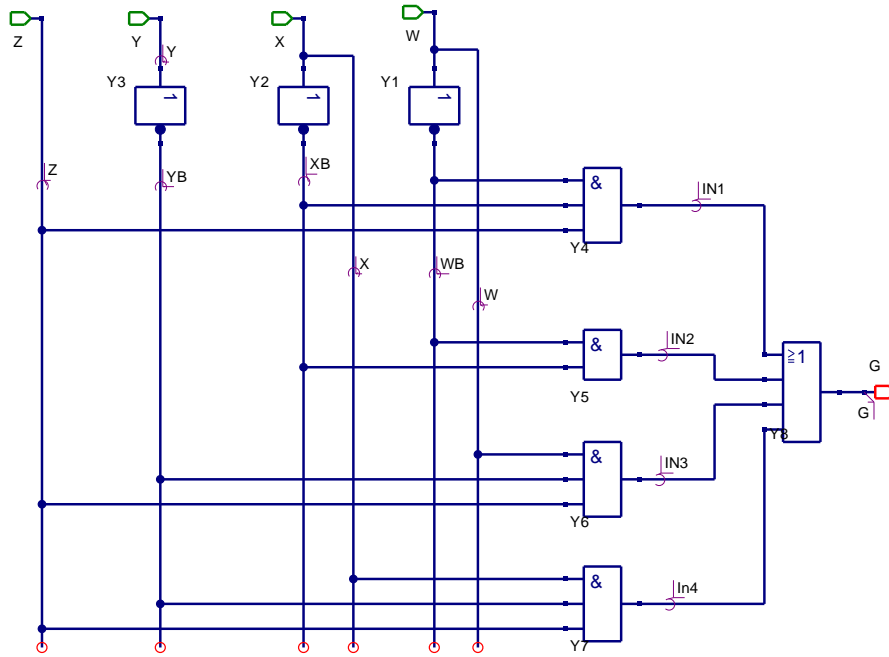


Figure 4: Combinational logic circuit with inputs W, X, Y, Z, and output G.

to the input of a digital clock. The specification for Gen4bit is given in the next section of these notes⁷. The test pattern waveform and output signal G are shown plotted as a function of time in Fig. 7.

⁷Subcircuit Gen4bit includes other nested subcircuits. Qucs 0.0.8 has a bug that causes VHDL compile errors with some configurations of nested subcircuits. This has been fixed in version 0.0.9.

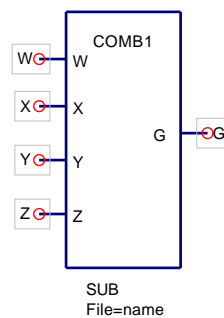


Figure 5: Qucs symbol for a logic circuit with inputs W, X, Y, Z, and output G.

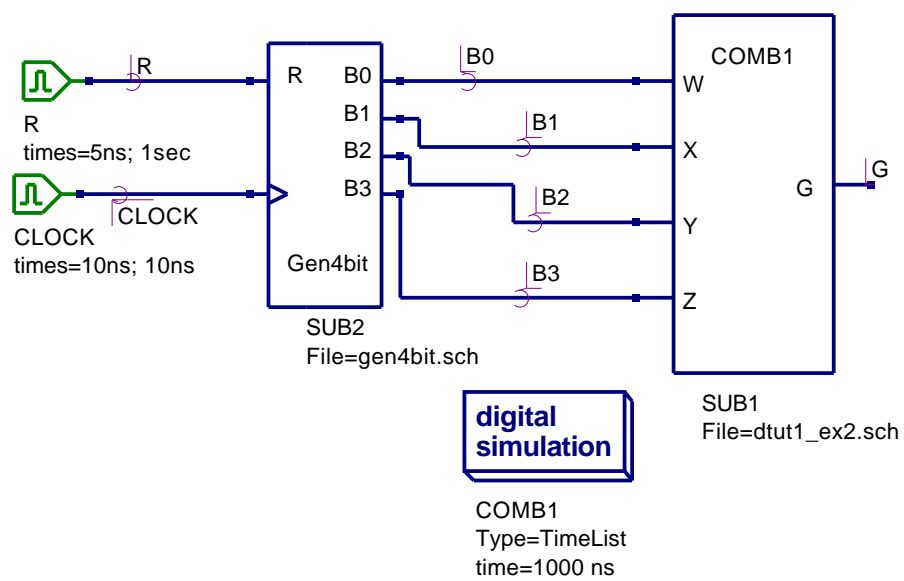


Figure 6: Test schematic for a logic circuit with inputs W, X, Y, Z, and output G.


 


Figure 7: Digital functional waveforms for a logic circuit with inputs W, X, Y, Z, and output G.


Building a digital component library

The Qucs graphical user interface includes good project handling features. Combining these features with the Qucs subcircuit capabilities provides all the tools required for the development of a library of common digital components. Such a library can be stored in a master project and the individual component files imported into other projects when required. Here are a few components that I developed during a recent series of tests aimed at detecting bugs in the VHDL code generated by Qucs.


Logic zero

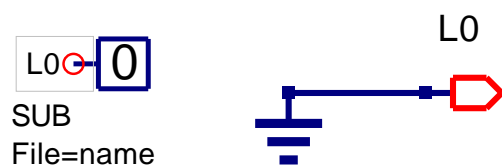


Logic one

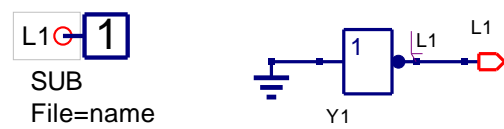


G2bit - 2 bit pattern generator

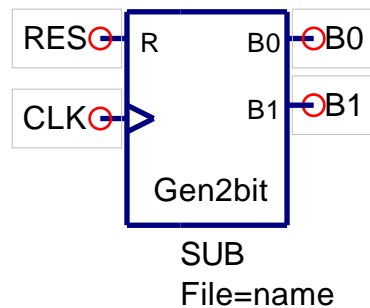


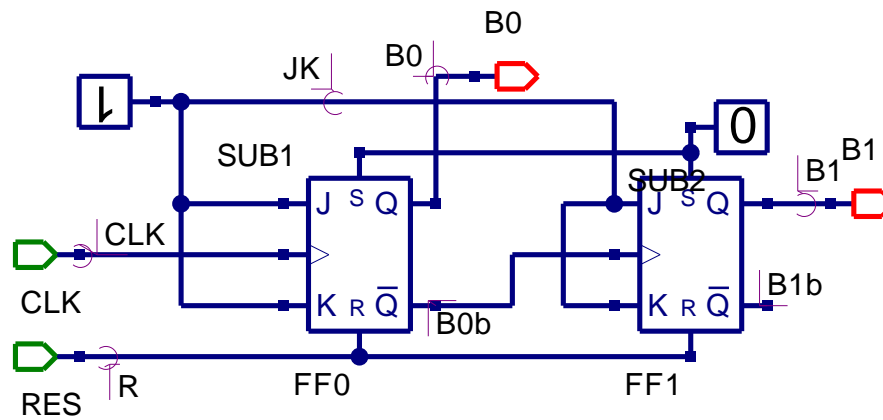

G4bit - 4 bit pattern generator


 


SUB
File=name

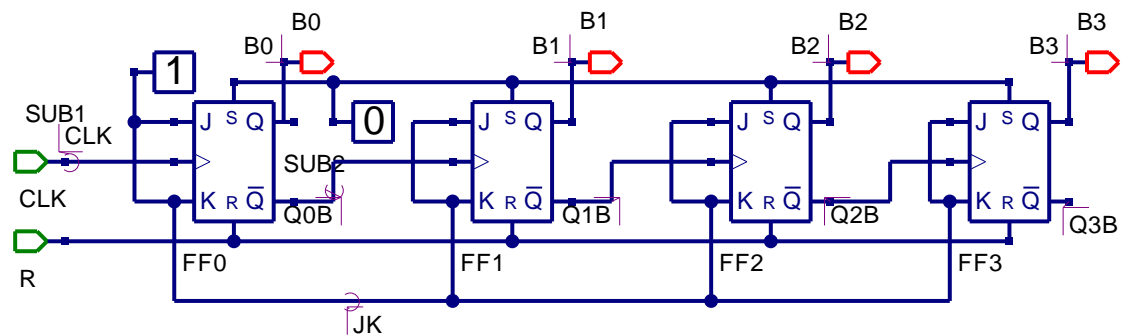


MUX2to1 - 2 input to 1 output multiplexer

EN	A	Y
1	X	L
0	0	D0
0	1	D1

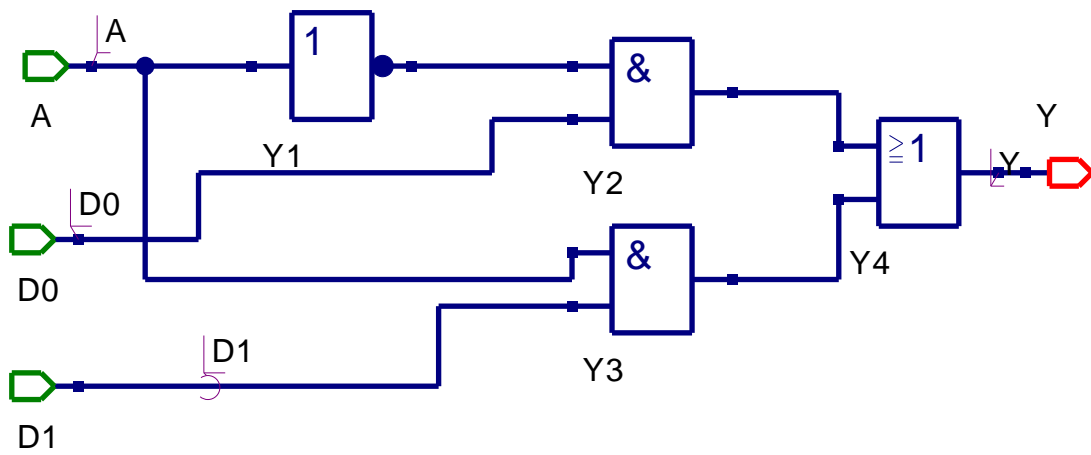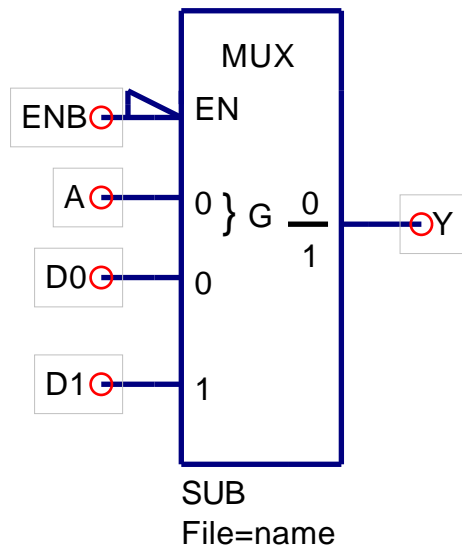


MUX4to1 - 4 input to 1 multiplexer



B	A	EN	Y
X	X	1	0
0	0	0	D0
0	1	0	D1
1	0	0	D2
1	1	0	D3

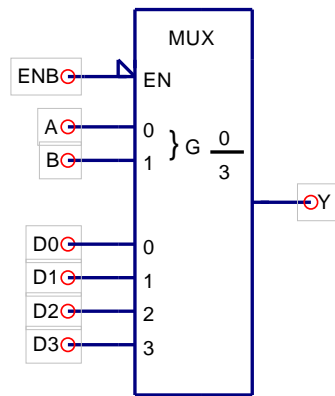

SUB
File=name

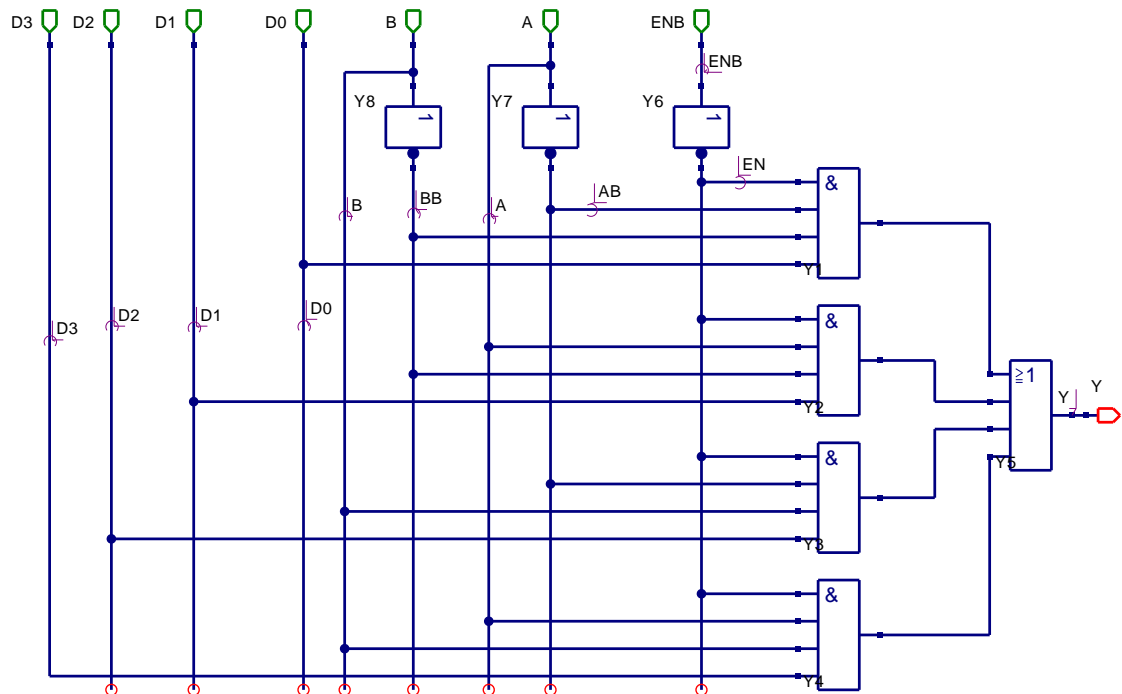

2 bit adder

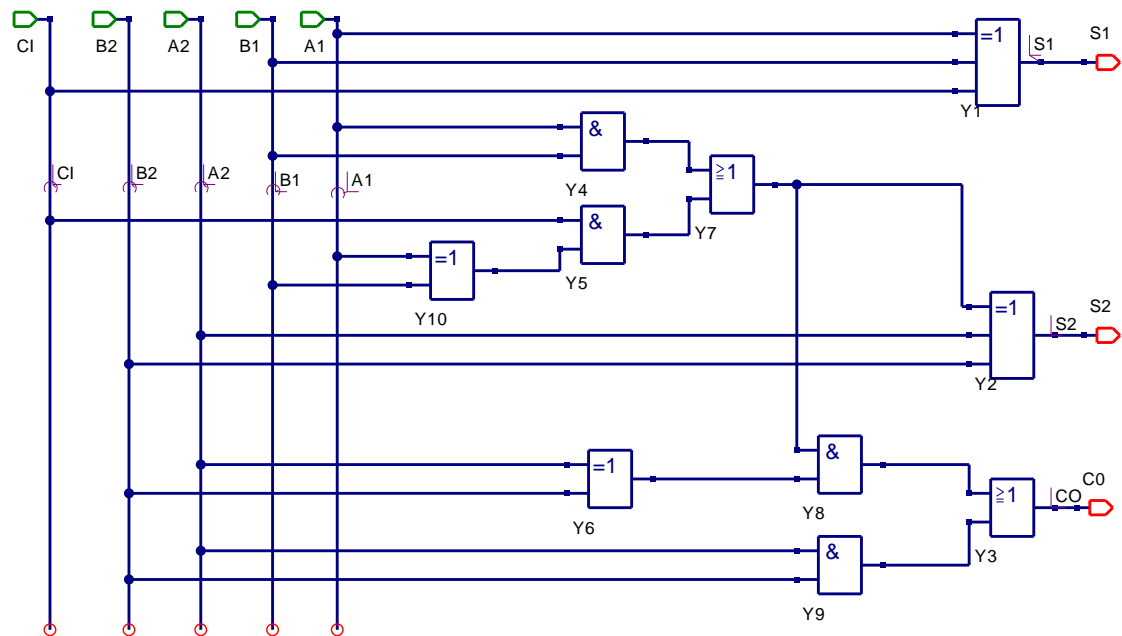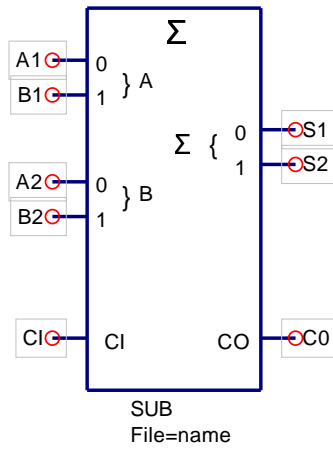

Subcircuit VHDL code generated by Qucs

Qucs generates a separate entity-architecture model for each subcircuit. These component definitions are compiled into the work library by FreeHDL. Here is the VHDL code from two of the previous examples.

Gen2bit

```

entity Sub_gen2bit is
  port (CLK: in bit;
        R: in bit;
        nnout_B0: out bit;
        nnout_B1: out bit);
end entity;
use work.all;
architecture Arch_Sub_gen2bit of Sub_gen2bit is
  signal B0b,
        B1b,
        JK,
        nnnet0,
        B0,
        B1 : bit;
begin
  FF0 : process (nnnet0, R, CLK)
  begin
    if (R='1') then B0 <= '0';
    elsif (nnnet0='1') then B0 <= '1';
    elsif (CLK='1' and CLK'event) then
      B0 <= (JK and not B0) or (not JK and B0);
    end if;
  end process;
  B0b <= not B0;

  FF1 : process (nnnet0, R, B0b)
  begin
    if (R='1') then B1 <= '0';
    elsif (nnnet0='1') then B1 <= '1';
    elsif (B0b='1' and B0b'event) then
      B1 <= (JK and not B1) or (not JK and B1);
    end if;
  end process;
  B1b <= not B1;

  SUB2: entity Sub_logic_zero port map (nnnet0);
  nnout_B0 <= B0 or '0';
  nnout_B1 <= B1 or '0';
  SUB1: entity Sub_Logic_one port map (JK);
end architecture;

```

2 bit adder

```

entity Sub_fadd_2bit is

```

```

    port (A1: in bit;
          B1: in bit;
          A2: in bit;
          B2: in bit;
          CI: in bit;
          nnout_S1: out bit;
          nnout_S2: out bit;
          nnout_CO: out bit);
end entity;
use work.all;
architecture Arch_Sub_fadd_2bit of Sub_fadd_2bit is
    signal nnnet0,
           nnnet1,
           nnnet2,
           nnnet3,
           nnnet4,
           nnnet5,
           nnnet6,
           S2,
           CO,
           S1 : bit;
begin
    S1 <= CI xor B1 xor A1;
    nnnet0 <= B2 xor A2;
    nnnet1 <= nnnet0 and nnnet2;
    nnnet3 <= B2 and A2;
    nnnet2 <= nnnet4 or nnnet5;
    nnnet4 <= nnnet6 and CI;
    nnnet5 <= B1 and A1;
    S2 <= B2 xor A2 xor nnnet2;
    CO <= nnnet3 or nnnet1;
    nnnet6 <= B1 xor A1;
    nnout_S2 <= S2 or '0';
    nnout_CO <= CO or '0';
    nnout_S1 <= S1 or '0';
end architecture;

```

Notes on subcircuit VHDL generation

- Qucs predefined digital components generate concurrent data flow signal statements or process statements.
- Previously defined subcircuit symbols generate VHDL port map statements.

- Type out entity port signals are prevented from being read as input signals by masking each output signal using the logic function **signal-name OR '0'**.⁸

- A VHDL

```
use work.all;
```

statement is included before each subcircuit architecture definition to ensure that FreeHDL can find any nested subcircuits⁹.

- The complete VHDL code file for a digital design is composed from an outer test bench entity-architecture model plus entity-architecture models for each subcircuit specified in the design,

Subcircuit nesting: A more complex design example

In theory there is no limit to the depth of subcircuit nesting allowed by Qucs. In practice most digital circuit schematics can be constructed with a maximum of four or five levels of design hierarchy. Figure 8 shows an example that was used to test Qucs subcircuit nesting performance. The design is a simple RTL function that uses a multiplexer to transfer data from one of two input registers to a single output register. The next section of these notes outlines in detail the specification of the subcircuits needed to build the RTL design. A set of sample simulation waveforms showing the register transfer operation are illustrated in Fig. 9.

⁸Attempting to read entity port signals of type out results in a VHDL compile error.

⁹Strictly speaking it should not be necessary to specifically state the use of the work library as this library is normally visible at all times when compiling entity-architecture models. However, at this stage in the development of FreeHDL it does appear that it is necessary when using the default FreeHDL VHDL library mapping.

4 bit RTL design



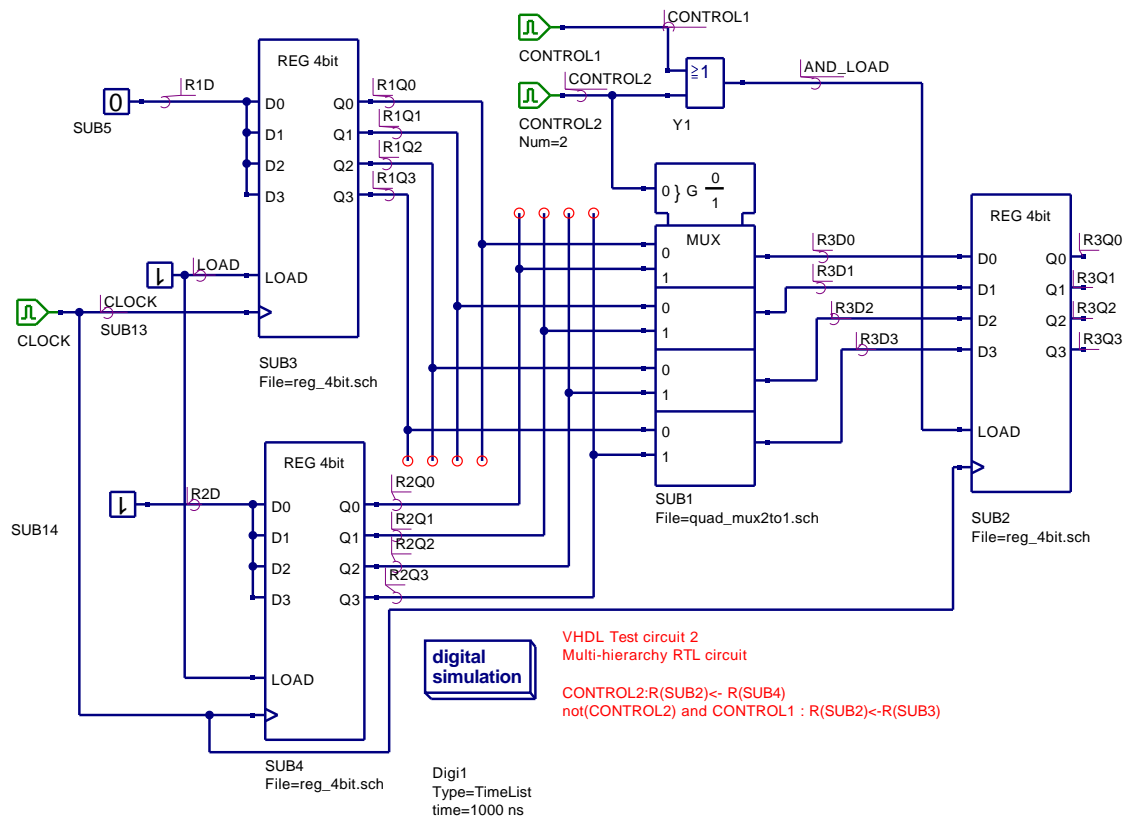



Figure 8: Top level schematic.

Reg4bit

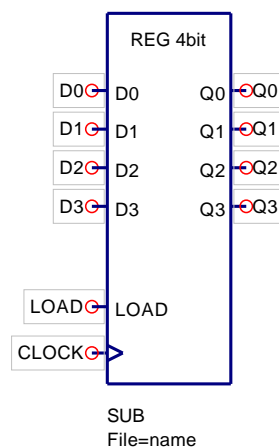


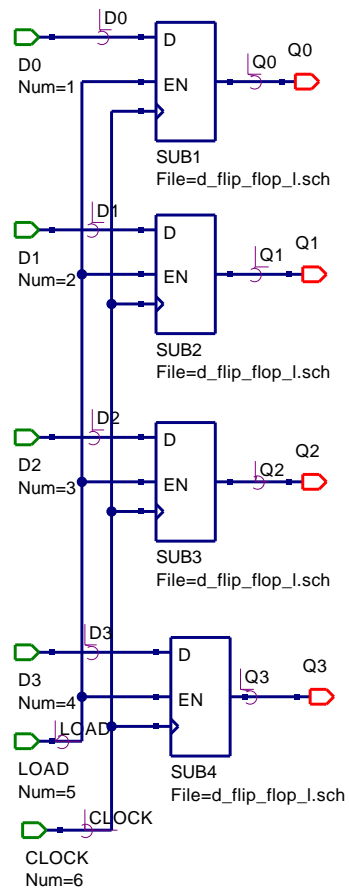


D flip-flop with load enable

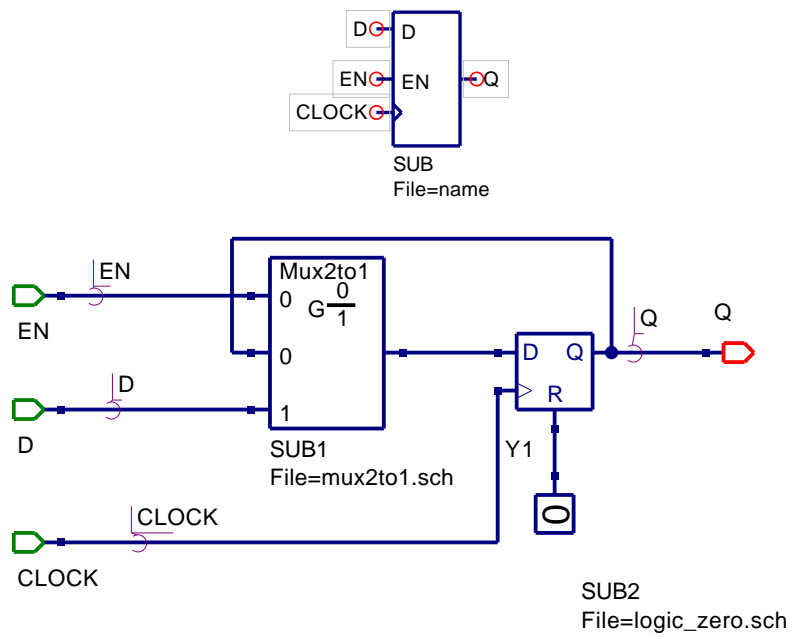

Mux2to1

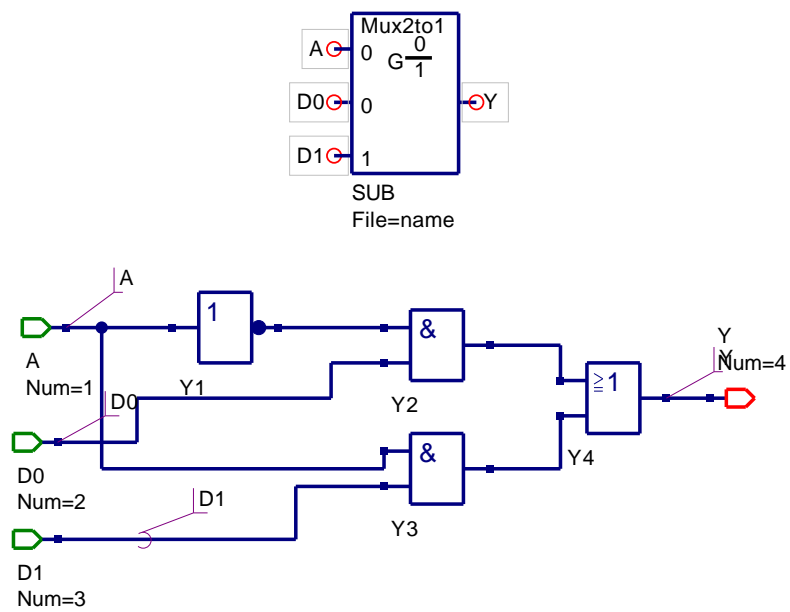

QuadMux

 

 


Figure 9: Sample simulation waveforms for RTL design.

Update number one: May 2006

Although it is only a short time since the first version of these digital tutorial notes was posted on the Qucs Sourceforge Web site, much has happened in the world of Qucs digital simulation. Bugs in the Qucs code have been found, and fixed, and a range of new features added to the software. These expand the power of Qucs digital simulation and give users a glimpse of how the package will evolve in the future. The purpose of these notes is firstly to update readers as to the changes to Qucs digital simulation and secondly to explain how to use the new Qucs features. Please note however, they are not intended to teach readers how to program using VHDL.¹⁰

Bugs, corrections and small changes to the Qucs digital simulation code

All the bugs reported in the first version of these notes have been corrected in the latest Qucs CVS code. These corrections are, of course, also included in Qucs release 0.0.9. During testing a number of other annoying, but significant, bugs have also been found and eliminated, these include

¹⁰A good introduction to the VHDL language and it's application in digital system design can be found in *Digital System Design using VHDL* by Charles H. Roth, Jr, PWS Publishing Company, 1997, ISBN 0-534-95099-X.

- Multiple input gates (three or more inputs) of types nand and nor failed at the FreeHDL compile stage due to an error in the VHDL code generated by Qucs.
- Signals names and, for example, component names constructed from a single letter that was an abbreviation for a physical unit failed to compile.
- Changing digital component time delays caused component connections on a schematic to be removed.
- GUI problems caused by errors in the symbol rotation and mirror code.
- Qucsconv code conversion errors caused the Qucs digital simulation cycle to fail before plotting TimeList waveforms.

A number of changes to either the VHDL code generated by Qucs or the schematic capture GUI have been introduced, these include

- The VHDL code generated by Qucs for the ground symbol has been changed from
`gnd <= gnd and '0';`
to
`gnd <= '0';`
- The symbol for digital inout ports has been changed from the analogue pin symbol to one that consists of the digital in and out pins drawn back-to-back. This reflects the bidirectional status of an inout port.

A more complete list of all the bug corrections and other program modifications can be found in the Qucs change log files.

New digital simulation features

The flow diagram illustrated in Fig. 10 shows a number of different simulation routes for a digital circuit under test. The Qucs digital simulation facilities have been improved to include direct simulation of VHDL testbench code and the simulation of circuit schematics that include digital components specified by VHDL entity-architecture models. The various combinations that users can adopt for Qucs digital circuit entry are as follows:

1. Schematic circuit entry using predefined digital component symbols, subcircuits generated using the same symbols and a copy of the digital simulation icon; this is the approach described in the first version of these tutorial notes.
2. Circuit entry identical to 1 plus symbols for digital components specified by VHDL entity-architecture models.
3. Circuit entry using the Qucs VHDL code editor. The text entered describes both the circuit under test and the test vectors needed to drive the circuit inputs during simulation.

Once the circuit under test has been entered into Qucs, clicking the Simulate menu button, or pressing key F2, starts the Qucs digital simulation process.

Limitations

Before describing the new digital simulation features it is important that readers understand the limitations that are inherent in the various digital simulation routes described in the last section and illustrated in the flow diagram shown in Fig. 10. Qucs schematic capture allows users to draw circuits consisting of predefined component symbols and subcircuit symbols. At this stage in the development of the GUI digital signals must be of type bit (as defined in the VHDL standard library - library STD in the FreeHDL package) where individual signals flow through a single wire. Qucs schematic drawing bus structures of VHDL type bit-vector, for example, have not been implemented yet. This implies that the device symbol port pins must represent single signals. Similarly the nets connecting pins on more than one device can only be single signal nets and not bus structures. It is anticipated that this will change in a future Qucs release.

Although the current release of FreeHDL is 0.0.1 the package implements a substantial subset of the entire VHDL language¹¹. The major features not supported by release 0.0.1 are:

- Shared variables.
- The following attributes; transaction, quiet, stable and delayed.
- User defined attributes.
- Groups.

¹¹A complete description of the 1987 and 1993 specifications of the VHDL language can be found in *The Designer's Guide to VHDL* by Peter J Ashenden, second edition 2002, Morgan Kaufmann Publishers, ISBN 1-55860-674-2.

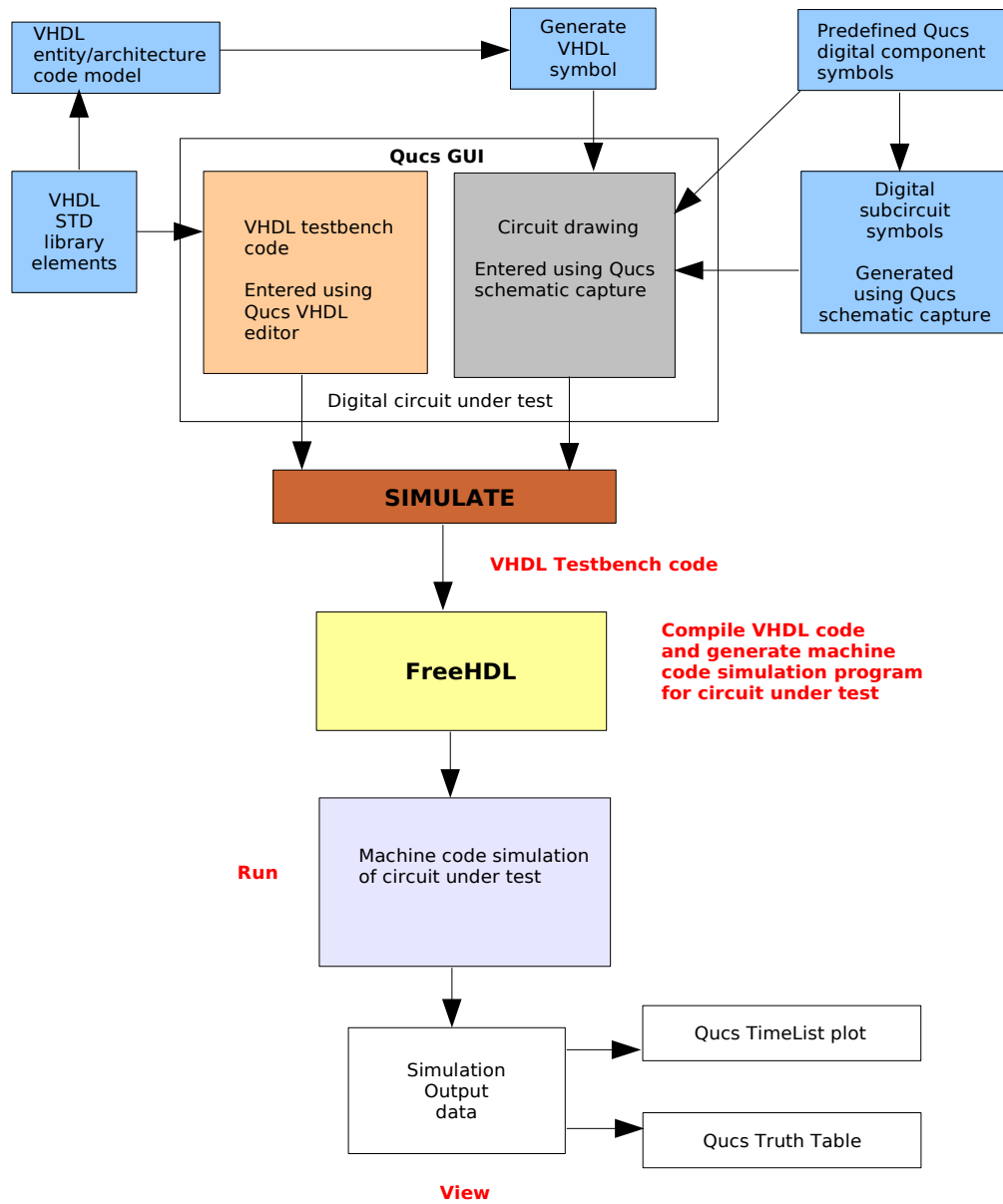


Figure 10: Flow diagram of Qucs digital simulation routes.

- Guarded signal assignments.
- Currently drivers cannot be switched off.

The Qucs TimeList plotting program uses signal data output by the machine code simulation program generated by the FreeHDL package¹². A current limitation of the TimeList plotting program is that it can only display signals of type bit. Bus signal waveforms cannot be displayed.

Given the above limitations it is therefore possible to write VHDL code that can be compiled by FreeHDL but will cause problems at either the schematic drawing or output waveform plotting stages in the Qucs simulation cycle. As Qucs develops it is expected that these limitations will be removed. On the subject of limitations one final point to note: FreeHDL can simulate circuits described by the data types and other features found in the

`IEEE.std_logic_1164`

library and other predefined libraries. However, at this stage in the development of the Qucs software only the VHDL standard library may be used, implying that data type bit must be used to represent logic signals.

Using the Qucs VHDL editor

Qucs release 0.0.9 includes a VHDL text editor¹³ that has all the usual edit features plus colour coding of the various VHDL language statements. One unusual feature of this editor is a zoom control that allows the text size to be increased or decreased in a similar way to the schematic drawing zoom. The VHDL editor is included in the Qucs package for two primary purposes, firstly for purely text file VHDL simulation¹⁴ and secondly for the development of VHDL entity-architecture models that can be linked to schematic capture symbols. The latter increases significantly the capabilities of the Qucs software in that it allows libraries of hand-crafted device models to be constructed. These new library devices will, given support by the general Qucs user community, greatly expand the potential use of the Qucs package. In this section the use of the VHDL text editor is demonstrated through a series of digital circuit simulation examples. The included VHDL listings indicate typical Qucs use of a number of the basic VHDL data types. The text also outlines any limitations imposed by Qucs.

¹²The machine code simulation program outputs signal data in VCD format. This is then converted to the Qucs TimeList data format by the `qucsconv` utility program.

¹³To launch the new VHDL editor click on the second icon from the left on the Qucs toolbar. It can also be activated using the key sequence Ctrl+Shift+V.

¹⁴This is still the preferred method amongst many experienced users of VHDL. However, the circuit schematic drawing approach does seem to be growing in popularity.

- Example 1: A sum of products (SOP) combinational digital circuit.

The Boolean equation¹⁵ for a SOP combinational circuit is:

$$f = \overline{W}.X.\overline{Y}.\overline{Z} + \overline{W}.\overline{X}.\overline{Y}.\overline{Z} + W.\overline{Y}.\overline{Z} + W.X.Y.Z$$

The VHDL code for a structural model of this combinational circuit and its associated testbench is given in the following listing.

```

— Qucs VHDL editor example 1
—
entity test_vector is — Test vector generator.
    port( z, y, x, w : out bit
        );
end entity test_vector;
—
architecture behavioural of test_vector is
begin
    pz : process is
        begin
            z <= '0' ; wait for 20 ns;
            z <= '1' ; wait for 20 ns;
        end process pz;
    py : process is
        begin
            y <= '0' ; wait for 40 ns;
            y <= '1' ; wait for 40 ns;
        end process py;
    px : process is
        begin
            x <= '0' ; wait for 80 ns;
            x <= '1' ; wait for 80 ns;
        end process px;
    pw : process is
        begin
            w <= '0' ; wait for 160 ns;
            w <= '1' ; wait for 160 ns;
        end process pw;
end architecture behavioural;
—
entity and4 is — 4 input and gate.

```

¹⁵The Boolean equation for function f has not been minimised. It is in a form derived directly from a truth table and is introduced purely as an example to demonstrate the use of the Qucs VHDL editor.

```

        port( in1, in2, in3, in4 : in bit;
              out1 : out bit
            );
end entity and4;
--
architecture dataflow of and4 is
begin
    out1 <= in1 and in2 and in3 and in4;
end architecture dataflow;
--
entity and3 is -- 3 input and gate.
    port( in1, in2, in3 : in bit;
          out1 : out bit
        );
end entity and3;
--
architecture dataflow of and3 is
begin
    out1 <= in1 and in2 and in3;
end architecture dataflow;
--
entity or4 is -- 4 input or gate.
    port( in1, in2, in3, in4 : in bit;
          out1 : out bit
        );
end entity or4;
--
architecture dataflow of or4 is
begin
    out1 <= in1 or in2 or in3 or in4;
end architecture dataflow;

entity inv is -- Inverter.
    port( in1 : in bit;
          out1 : out bit
        );
end entity inv;
--
architecture dataflow of inv is
begin
    out1 <= not in1;
end architecture dataflow;
--

```



```

entity testbench is — Test bench outer entity wrapper.
end entity testbench;

—

library work;
use work.all;

—

architecture structural of testbench is — Testbench architecture.
signal b0, b1, b2, b3, zb, yb, xb, wb, a, b, c, d, f : bit;
begin
    d1 : entity test_vector port map(b0, b1, b2, b3);
    d2 : entity inv port map(b0, wb);
    d3 : entity inv port map(b1, xb);
    d4 : entity inv port map(b2, yb);
    d5 : entity inv port map(b3, zb);
    d6 : entity and4 port map(zb, yb, b1, wb, a);
    d7 : entity and4 port map(zb, yb, xb, wb, b);
    d8 : entity and3 port map(zb, yb, b0, c);
    d9 : entity and4 port map(b0, b1, b2, b3, d);
    d10 : entity or4 port map(a, b, c, d, f);
end architecture structural;

```

On entry of this code into the Qucs VHDL text editor the text is colour coded. Unfortunately, the colour coding is lost when printed, or pasted into a word processor, or a layout package like LaTeX. The structure of the VHDL listing follows the normal convention for text based VHDL simulation. All component entity-architecture models must be defined before they are referenced in other component models. The simulation test bench must be the last entity-architecture model in the VHDL listing. During the VHDL compile phase FreeHDL compiles the component entity-architecture models to the work library¹⁶. These compiled models are then made available to the simulation test bench through the use of the VHDL ***use*** statement inserted in the listing prior to the testbench architecture statement. Once the VHDL listing for the simulation has been typed into the Qucs VHDL code editor, pressing key F2 starts the simulation process. The simulation duration can be set using the Document Settings in the File dropdown menu (or by pressing the Ctrl+. keys). Any VHDL syntax errors, or indeed typos, are written to file and can be viewed by pressing key F5. Obviously if errors are reported these need to be corrected using the VHDL text editor and the simulation cycle restarted. A typical TimeList output for editor example 1 is shown in

¹⁶In most VHDL implementations library work is always visible and there is no requirement to make it visible by using the library and use statements. However, FreeHDL appears to need these statements at the linking phase otherwise the VHDL compiler fails.

Fig. 11.

 


Figure 11: Sample simulation waveforms for VHDL editor example 1 design.

- Example 2: VHDL editor example 1 modelled using dataflow VHDL statements.

The VHDL code for the second example is given in the next listing. The VHDL style chosen to model the circuit is based on VHDL dataflow concurrent signal assignments. The input text vectors are generated using a simple state machine rather than separate process statements. The test vector generator port specification uses entirely single signal bit types and can be easily interfaced, without problems, to other components connected on a Qucs schematic diagram. The procedure for generating schematic capture component symbols from entity - architecture models is introduced in a later section of these notes. The use of bit vector bus constructions is also illustrated in this example. Qucs allows the use of bit vectors as signals or variables in VHDL models provided all signals in the port statement of entity declaration are of type bit only.¹⁷ A typical TimeList output for editor example 2 is shown in Fig. 12.

— *Qucs VHDL editor example 2*

```

entity test_vector_a is
    port( RESET, CLOCK : in bit;
          B0, B1, B2, B3 : out bit
    );
end entity test_vector_a;

architecture behavioural of test_vector_a is
    signal present_state, next_state : bit_vector(3 downto 0):="1111";
begin

```

¹⁷This is a restriction of Qucs 0.0.9 and will be removed in a later release of the package. Also note signals of type bit vector that are declared in architecture definitions are listed in the TimeList plot signal dialogue. However, a text message saying no data results if an attempt is made to display them. Again this limitation will be removed in a later release of Qucs.

```

—
p1 : process(CLOCK ) is
    begin
        if (CLOCK'event and CLOCK='1') then
            present_state <= next_state;
        end if;
    end process p1;
—
p2 : process(RESET,  present_state) is
    begin
        if (RESET = '1' ) then next_state <= "1111";
        end if;
        case present_state is
            when "0000" => next_state <= "0001";
            when "0001" => next_state <= "0010";
            when "0010" => next_state <= "0011";
            when "0011" => next_state <= "0100";
            when "0100" => next_state <= "0101";
            when "0101" => next_state <= "0110";
            when "0110" => next_state <= "0111";
            when "0111" => next_state <= "1000";
            when "1000" => next_state <= "1001";
            when "1001" => next_state <= "1010";
            when "1010" => next_state <= "1011";
            when "1011" => next_state <= "1100";
            when "1100" => next_state <= "1101";
            when "1101" => next_state <= "1110";
            when "1110" => next_state <= "1111";
            when "1111" => next_state <= "0000";
        end case;
        B3 <= next_state(3); B2 <= next_state(2);
        B1 <= next_state(1); B0 <= next_state(0);
    end process p2;
end architecture behavioural;
—
library work;
use work.all;
—
entity testbench is
end entity testbench;
—
architecture dataflow of testbench is
    signal  reset , clk , b0 , b1 , b2 , b3 , zb : bit;

```

```

signal  yb, xb, wb,a, b, c, d, f : bit;
begin
p1 : process is
    begin
        clk <= '0'; wait for 10 ns;
        clk <= '1'; wait for 10 ns;
    end process p1;

—
p2 : process is
    begin
        reset <= '1'; wait for 10 ns;
        reset <= '0'; wait for 2000 ns;
    end process p2;

—
d1 : entity test_vector_a port map(reset , clk , b0, b1, b2, b3);
—
—    Data flow model of combinational circuit
wb <= not b0;  xb  <= not b1;  yb  <= not b2;  zb <= not b3;
a <= (wb and b1) and (yb and zb);
b <= (wb and xb) and (yb and zb);
c <= b0 and (yb and zb);
d <= (b0 and b1) and (b2 and b3);
f  <= a or b or c or d;
end architecture dataflow;

```

 


Figure 12: Sample simulation waveforms for VHDL editor example 2 design.

- Example 3: VHDL editor example 1 modelled using VHDL process statements and variables.

The VHDL code for the third example is given in the listing at the end of this paragraph. In this example the use of VHDL variables is illustrated. The VHDL code for the vector generator is a little unusual in that rather than using the traditional two process design employing signals, a single process statement employing variables undertakes both the calculation of

the next state data and the transfer of the next state information to the present state. This approach is necessary because FreeHDL does not allow shared variables. Once again in this example only single bit data is passed via the entity statement to the device under test. The device under test is represented by a truth table encoded in a process statement. This is not the most elegant code but it does serve the purpose of demonstrating the use of different VHDL constructions and data types in Qucs digital simulation. A typical TimeList plot for VHDL editor example 3 is shown in Fig. 13. Comparison of the three output plots for the VHDL editor examples indicates that all the simulation results are very similar with some slight differences in the start up phase following the RESET pulse changing from logic '1' to logic '0'. This is probably an effect due to the different initialisation sequences for each of the test vector models.

— *Qucs VHDL editor example 3*

```

entity test_vector_b is
    port( RESET, CLOCK : in bit;
          B0, B1, B2, B3 : out bit
    );
end entity test_vector_b;

architecture behavioural of test_vector_b is
begin
p1 : process(RESET, CLOCK) is
    variable present_state, next_state :
        bit_vector(3 downto 0):="0000";
    begin
        if (RESET = '1' ) then next_state := "0000";
        elsif (CLOCK'event and CLOCK='1') then
            present_state := next_state;
        case present_state is
            when "0000" => next_state := "0001";
            when "0001" => next_state := "0010";
            when "0010" => next_state := "0011";
            when "0011" => next_state := "0100";
            when "0100" => next_state := "0101";
            when "0101" => next_state := "0110";
            when "0110" => next_state := "0111";
            when "0111" => next_state := "1000";
            when "1000" => next_state := "1001";
            when "1001" => next_state := "1010";
            when "1010" => next_state := "1011";

```

```

        when "1011" => next_state := "1100";
        when "1100" => next_state := "1101";
        when "1101" => next_state := "1110";
        when "1110" => next_state := "1111";
        when "1111" => next_state := "0000";
    end case;
end if;
B3 <= next_state(3); B2 <= next_state(2);
B1 <= next_state(1); B0 <= next_state(0);
end process p1;
end architecture behavioural;
--
library work;
use work.all;
--
entity testbench is
end entity testbench;
--
architecture dataflow of testbench is
    signal reset, clk, b0, b1, b2, b3, f : bit;
begin
    p1 : process is
        begin
            clk <= '0'; wait for 10 ns;
            clk <= '1'; wait for 10 ns;
        end process p1;
    --
    p2 : process is
        begin
            reset <= '1'; wait for 10 ns;
            reset <= '0'; wait for 2000 ns;
        end process p2;
    --
    d1 : entity test_vector_b port map(reset, clk, b0, b1, b2, b3);
    --
    -- Behavioural model of combinational circuit
    p3: process(b3, b2, b1, b0) is
        variable SEL : bit_vector (3 downto 0);
        begin
            SEL := b3&b2&b1&b0 ;
            if (SEL = "0010") then f <= '1';
            elsif (SEL = "0000") then f <= '1';
            elsif (SEL = "1111") then f <= '1';

```

```

        elsif (SEL = "0001") then f <= '1';
        elsif (SEL = "0011") then f <= '1';
        else f <= '0';
        end if;
    end process p3;
end architecture dataflow;

```

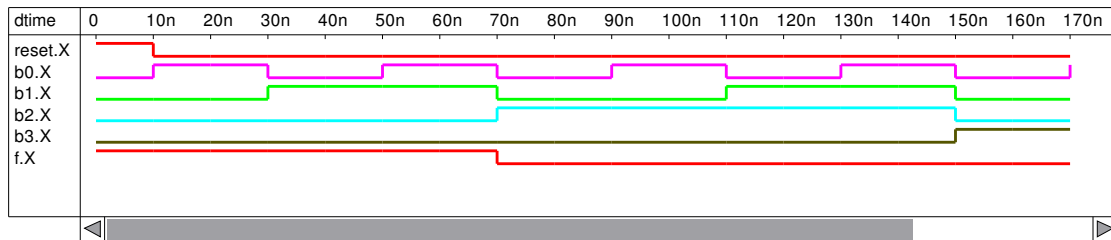


Figure 13: Sample simulation waveforms for VHDL editor example 3 design.

Linking VHDL entity-architecture models to Qucs schematic device symbols

VHDL was originally developed as a hardware description language for specifying digital systems. Indeed many engineers still prefer to describe digital systems entirely in VHDL statements rather than use schematic drawings. Once written VHDL code is saved as a text file and becomes the input data for a VHDL compiler/simulation package. Through popular demand a number of digital synthesis/simulator CAD tools¹⁸ have started to include a facility that links VHDL model code to a schematic capture symbol. It is then, of course, possible to use a schematic diagram as the main entry media¹⁹ when designing and simulating a digital design. Qucs release 0.0.9 has such a facility, allowing VHDL code models to be linked to schematic symbols. When drawing digital design schematics, these user defined symbols may be mixed with the Qucs predefined digital symbols and other user defined subcircuit symbols. The process for linking VHDL code to Qucs schematic drawing symbols is straightforward and will be illustrated in these notes through two examples.

- Example 4: A 4 bit test vector pattern generator.

¹⁸See for example the XILINX, WebPACK software at http://www.xilinx.com/ise/logic_design_prod/webpack.htm.

¹⁹Please note that at the start of the VHDL simulation process schematic drawings are converted into a VHDL text file.

Shown in Table 4 is the VHDL entity-architecture model listing for a 4 bit binary pattern generator. The VHDL code is identical to the test vector code introduced in the third VHDL editor example. After entering the VHDL entity-architecture model code using the Qucs VHDL editor the finished text is saved in a file with a suitable name and file extension vhd. Qucs then lists the model under the VHDL project category. Simply clicking on a model name in the VHDL category, with the left hand mouse button, then moving the mouse pointer to a suitable position on a schematic, causes Qucs to move a symbol that represents the model onto the schematic drawing sheet. Placement of the symbol at the position located by the mouse pointer is achieved by clicking the left hand mouse button. The procedure is identical to that used to select and place the Qucs predefined symbols on a schematic drawing. Qucs automatically generates a rectangular symbol with a name called VHDL that has the same number of pins as the port statement listed in the VHDL model entity statement. Each of the pins is given a name that corresponds to a name in the entity statement. Qucs fixes the order of the pins on the generated symbol. It appears that it is not possible to edit this symbol. However, subcircuit in, out or inout port symbols can be attached to symbol VHDL and a user edited symbol generated. Fig. 14 shows the Qucs generated VHDL symbol with attached ports for the model listed in Table 4. The edited symbol for the 4 bit binary pattern generator is illustrated in Fig. 15. Notice that in Fig. 15 the order of the pins has been changed to reflect the natural order for a device with its input pins on the left and output pins on the right. VHDL model symbols can also be generated by placing the VHDL file component, this is located in the digital components viewlist, on a schematic. On editing the VHDL file name property of this device to the name of a VHDL entity-architecture model file, Qucs automatically generates a VHDL symbol. Defining your own symbol then proceeds in a similar fashion to the way described above.

- Example 5: A 4 bit full adder.

VHDL model symbols may be combined with either the Qucs predefined digital component symbols or other subcircuit symbols. In this example a VHDL model for a simple one bit full adder is connected four times in a serial fashion to form a 4 bit full adder. The VHDL model code for a simple one bit full adder is given in Table 5. The associated symbol diagrams for the one bit full adder are illustrated in Fig. 16 and Fig. 17.


```

entity patgen_4bit is
    port( RESET, CLOCK : in bit;
          B0, B1, B2, B3 : out bit
    );
end entity patgen_4bit;
—
architecture behavioural of patgen_4bit is
begin
p1 : process(RESET, CLOCK) is
    variable present_state, next_state :
        bit_vector(3 downto 0):="0000";
begin
    if (RESET = '1' ) then next_state := "0000";
    elsif (CLOCK'event and CLOCK='1') then
        present_state := next_state;
        case present_state is
            when "0000" => next_state := "0001";
            when "0001" => next_state := "0010";
            when "0010" => next_state := "0011";
            when "0011" => next_state := "0100";
            when "0100" => next_state := "0101";
            when "0101" => next_state := "0110";
            when "0110" => next_state := "0111";
            when "0111" => next_state := "1000";
            when "1000" => next_state := "1001";
            when "1001" => next_state := "1010";
            when "1010" => next_state := "1011";
            when "1011" => next_state := "1100";
            when "1100" => next_state := "1101";
            when "1101" => next_state := "1110";
            when "1110" => next_state := "1111";
            when "1111" => next_state := "0000";
        end case;
    end if;
    B3 <= next_state(3); B2 <= next_state(2);
    B1 <= next_state(1); B0 <= next_state(0);
end process p1;
end architecture behavioural;

```

Table 4: VHDL code for a 4 bit pattern generator.

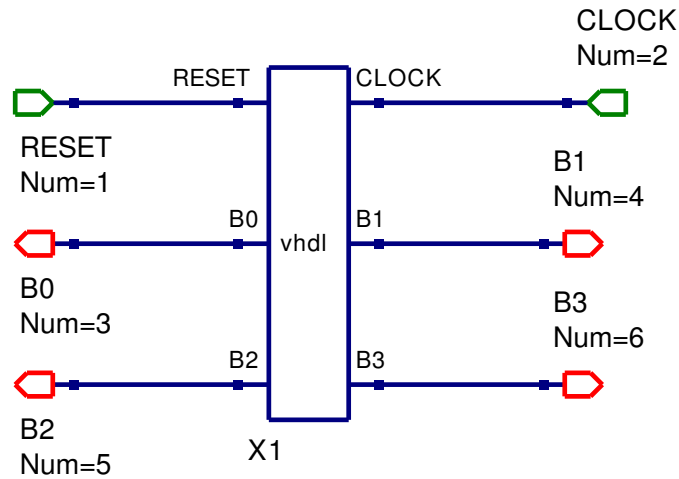


Figure 14: Qucs generated VHDL symbol with subcircuit ports for test pattern generator.

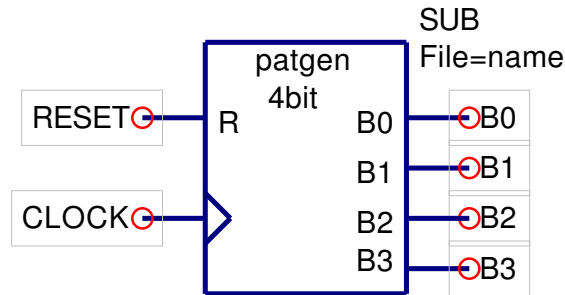


Figure 15: User defined 4 bit pattern generator symbol.

```

— Full adder — 1 bit
entity fulladder is
    port (a, b, cin : in bit;
          sum, cout : out bit
    );
end entity fulladder;

—
architecture dataflow of fulladder is
begin
    sum <= (a xor b) xor cin;
    cout <= (a and b) or (a and cin) or (b and cin);
end architecture dataflow;

```

Table 5: VHDL code for a 1 bit full adder.

 


Figure 16: Qucs generated VHDL symbol with subcircuit ports for one bit full adder.

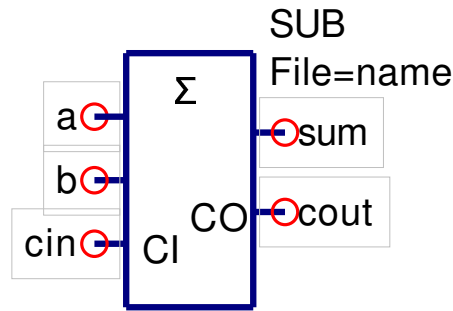


Figure 17: User defined one bit full symbol.

Figure 18 shows the schematic for a simple 4 bit ripple adder. The corresponding user defined symbol for the 4 bit full adder is given in Fig. 19.

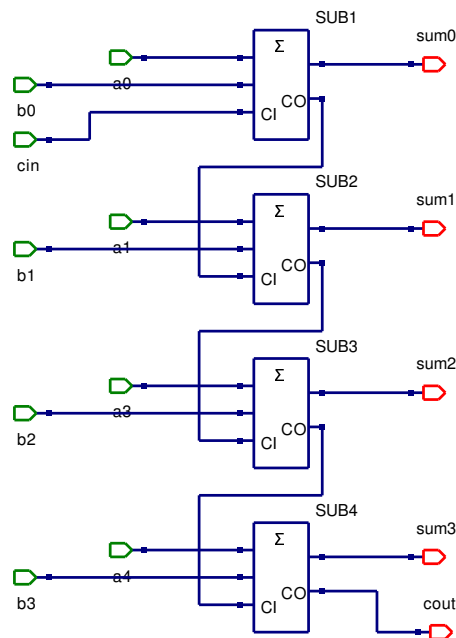


Figure 18: 4 bit full adder schematic.

Generating VHDL code from Qucs schematic drawings

Pressing key F2 causes Qucs to simulate the design entered by the Qucs user. The input data for a simulation is either a VHDL text file, saved from the VHDL text editor, or a VHDL code file generated by Qucs using the information encoded on a schematic drawing. In this section of these tutorial notes a larger design is introduced and the resulting VHDL code and simulation results are discussed.

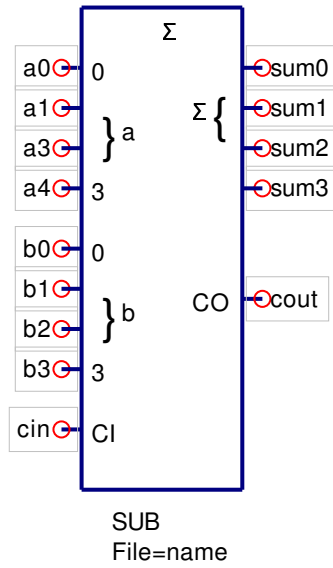


Figure 19: User defined 4 bit full adder symbol.

				b3	b2	b1	b0
				a3	a2	a1	a0
				a0b3	a0b2	a0b1	a0b0
			a1b3	a1b2	a1b1	a1b0	
		a2b3	a2b2	a2b1	a2b0		
	a3b3	a3b2	a3b1	a3b0			
r7	r6	r5	r4	r3	r2	r1	r0

Table 6: Product table for a 4 bit by 4 bit combinational multiplier.

The example chosen for this purpose is a 4 bit by 4 bit combinational digital multiplier. Both the 4 bit pattern generator and the 4 bit full adder outlined in the last section form part of the central core of the 4 bit multiplier design and it's associated testbench. Table 6 shows the multiplication product table for a 4 bit by 4 bit combinational binary multiplier. Inputs to the device are binary bits a3 a2 a1 a0 and b3 b2 b1 b0. The 4 by 4 multiplier device requires 16 and gates (to generate the multiplier product terms), three four bit full adders (to sum the output r terms) and two 4 bit pattern generators to test the 256 possible input states. The multiplier output is represented in Table 6 by r7 r6 r5 r4 r3 r2 r1 and r0. The circuit schematic for the 4 bit by 4 bit multiplier and test bench are given in Fig. 20.

The VHDL code for this example is presented in the following listing. This listing

was generated by Qucs²⁰. A small section of the TimeList waveform plot for the digital multiplier is shown in Fig. 21. At 1.74 micro seconds input a is "0101", input b is "0111" and the output r is "00100011" which is 35 in decimal. Taking a few random checks of the simulation results indicates that the 4 bit by 4 bit multiplier design works correctly. Notice that the VHDL code generated by Qucs for the 4 bit multiplier does not contain any propagation delay timing data. This could be added to the and gates, if required. However, at this stage in the development of Qucs digital simulation passing timing data, and other parameters, from device symbols generated from VHDL models has not been implemented yet. The use of VHDL generics is an obvious way this could be done. Generics are allowed, of course, in text based VHDL simulations.

²⁰Some readers will have noticed that the naming scheme for internal signal nets is different in the multiplier VHDL listing when compared to the VHDL listings in the first version of these notes. Towards the end of the 0.0.9 development phase the naming convention employed by Qucs was changed to give a more flexible structure.

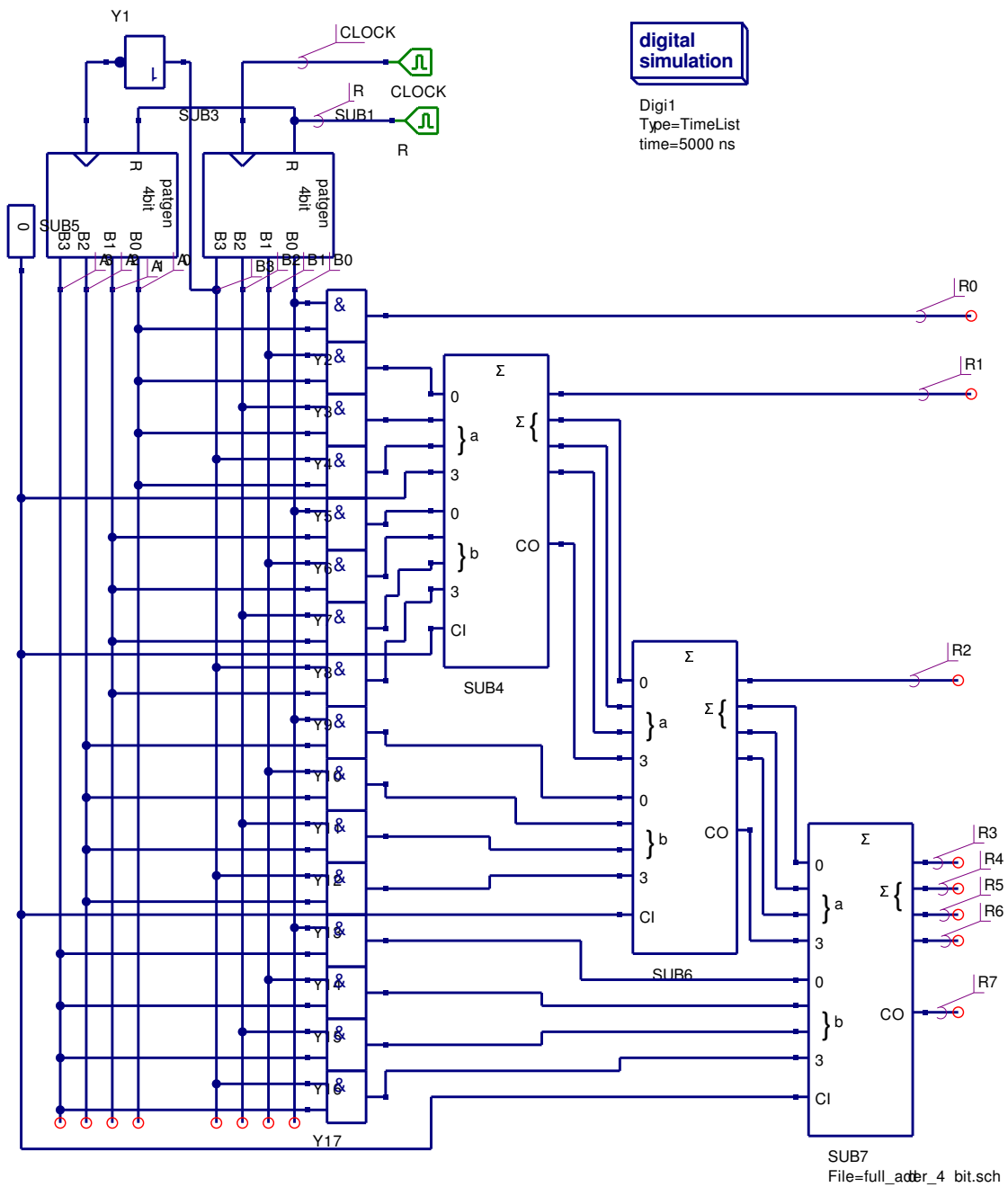


Figure 20: A 4 bit by 4 bit combinational digital multiplier.

```

— Qucs 0.0.9
— /mnt/hda2/vhdl-comp-lib-prj/multiplier_4bx4bit.sch

entity patgen_4bit is
    port( RESET, CLOCK : in bit;
          B0, B1, B2, B3 : out bit
        );
end entity patgen_4bit;
—
architecture behavioural of patgen_4bit is
begin
    p1 : process(RESET, CLOCK) is
        variable present_state, next_state :
            bit_vector(3 downto 0) := "0000";
    begin
        if (RESET = '1' ) then next_state := "0000";
        elsif (CLOCK'event and CLOCK='1') then
            present_state := next_state;
            case present_state is
                when "0000" => next_state := "0001";
                when "0001" => next_state := "0010";
                when "0010" => next_state := "0011";
                when "0011" => next_state := "0100";
                when "0100" => next_state := "0101";
                when "0101" => next_state := "0110";
                when "0110" => next_state := "0111";
                when "0111" => next_state := "1000";
                when "1000" => next_state := "1001";
                when "1001" => next_state := "1010";
                when "1010" => next_state := "1011";
                when "1011" => next_state := "1100";
                when "1100" => next_state := "1101";
                when "1101" => next_state := "1110";
                when "1110" => next_state := "1111";
                when "1111" => next_state := "0000";
            end case;
        end if;
        B3 <= next_state(3); B2 <= next_state(2);
        B1 <= next_state(1); B0 <= next_state(0);
    end process p1;
end architecture behavioural;

entity Sub_patgen_4bit is

```



```

    port (net_net0: in bit;
          net_net5: in bit;
          net_outnet_net1: out bit;
          net_outnet_net3: out bit;
          net_outnet_net2: out bit;
          net_outnet_net4: out bit);
end entity;
use work.all;
architecture Arch_Sub_patgen_4bit of Sub_patgen_4bit is
    signal net_net1,
           net_net2,
           net_net3,
           net_net4 : bit;
begin
    net_outnet_net1 <= net_net1 or '0';
    net_outnet_net2 <= net_net2 or '0';
    net_outnet_net3 <= net_net3 or '0';
    net_outnet_net4 <= net_net4 or '0';
    X1: entity patgen_4bit port map (net_net0, net_net5,
                                     net_net1, net_net3, net_net2, net_net4);
end architecture;

```

```

-- logic_zero.vhdl
entity logic_zero is
    port( Y : out bit
          );
end entity logic_zero;
--
architecture dataflow of logic_zero is
begin
    Y <= '0';
end architecture dataflow;

```

```

entity Sub_logic_zero is
    port (net_outnetY: out bit);
end entity;
use work.all;
architecture Arch_Sub_logic_zero of Sub_logic_zero is
    signal netY : bit;
begin
    X1: entity logic_zero port map (netY);

```

```

    net_outnetY <= netY or '0';
end architecture;

-- Full adder - 1 bit
entity fulladder is
    port (a, b, cin : in bit;
          sum, cout : out bit
        );
end entity fulladder;

--
architecture dataflow of fulladder is
begin
    sum <= (a xor b) xor cin;
    cout <= (a and b) or (a and cin) or (b and cin);
end architecture dataflow;

entity Sub_full_adder_1bit is
    port (net_net0: in bit;
          net_net1: in bit;
          net_net2: in bit;
          net_outnet_net3: out bit;
          net_outnet_net4: out bit);
end entity;
use work.all;
architecture Arch_Sub_full_adder_1bit of Sub_full_adder_1bit is
    signal net_net3,
           net_net4 : bit;
begin
    X1: entity fulladder port map (net_net0, net_net1,
                                   net_net2, net_net3, net_net4);
    net_outnet_net3 <= net_net3 or '0';
    net_outnet_net4 <= net_net4 or '0';
end architecture;

entity Sub_full_adder_4bit is
    port (net_net0: in bit;
          net_net1: in bit;
          net_net2: in bit;
          net_net3: in bit;
          net_net4: in bit;

```

```

        net_net5: in bit;
        net_net6: in bit;
        net_net13: in bit;
        net_net7: in bit;
        net_outnet_net8: out bit;
        net_outnet_net9: out bit;
        net_outnet_net10: out bit;
        net_outnet_net11: out bit;
        net_outnet_net12: out bit);
end entity;
use work.all;
architecture Arch_Sub_full_adder_4bit of Sub_full_adder_4bit is
    signal net_net14,
           net_net15,
           net_net16,
           net_net8,
           net_net9,
           net_net10,
           net_net11,
           net_net12 : bit;
begin
    net_outnet_net8 <= net_net8 or '0';
    net_outnet_net9 <= net_net9 or '0';
    net_outnet_net10 <= net_net10 or '0';
    net_outnet_net11 <= net_net11 or '0';
    net_outnet_net12 <= net_net12 or '0';
    SUB4: entity Sub_full_adder_1bit port map (net_net3, net_net13,
        net_net14, net_net11, net_net12);
    SUB3: entity Sub_full_adder_1bit port map (net_net2, net_net6,
        net_net15, net_net10, net_net14);
    SUB2: entity Sub_full_adder_1bit port map (net_net1, net_net5,
        net_net16, net_net9, net_net15);
    SUB1: entity Sub_full_adder_1bit port map (net_net0, net_net4,
        net_net7, net_net8, net_net16);
end architecture;

entity TestBench is
end entity;
use work.all;

architecture Arch_TestBench of TestBench is
    signal netA0, netA1, netA2, netA3, netR, netB0,
           netB1, netB2, netB3, netR0, netR1, netR2,

```

```

    netR3, netR4, netR5, netR6, netR7, netCLOCK,
    net_net0, net_net1, net_net2, net_net3, net_net4,
    net_net5, net_net6, net_net7, net_net8, net_net9,
    net_net10, net_net11, net_net12, net_net13, net_net14,
    net_net15, net_net16, net_net17, net_net18, net_net19,
    net_net20, net_net21, net_net22, net_net23,
    net_net24 : bit;
begin
    SUB3: entity Sub_patgen_4bit port map (netR, net_net0,
        netA0, netA1, netA2, netA3);
    SUB1: entity Sub_patgen_4bit port map (netR, netCLOCK,
        netB0, netB1, netB2, netB3);

    R: process
    begin
        netR <= '1'; wait for 10 ns;
        netR <= '0'; wait for 2000 ns;
    end process;

    CLOCK: process
    begin
        netCLOCK <= '0'; wait for 10 ns;
        netCLOCK <= '1'; wait for 10 ns;
    end process;

    net_net0 <= not netB3;
    netR0 <= netA0 and netB0;
    net_net1 <= netA0 and netB1;
    net_net2 <= netA0 and netB2;
    net_net3 <= netA0 and netB3;
    SUB5: entity Sub_logic_zero port map (net_net4);
    net_net5 <= netA1 and netB0;
    net_net6 <= netA1 and netB1;
    net_net7 <= netA1 and netB2;
    net_net8 <= netA1 and netB3;
    net_net9 <= netA2 and netB0;
    net_net10 <= netA2 and netB1;
    net_net11 <= netA2 and netB2;
    net_net12 <= netA2 and netB3;
    SUB4: entity Sub_full_adder_4bit port map (net_net1, net_net2,
        net_net3, net_net4, net_net5, net_net6, net_net7,
        net_net8, net_net4, netR1, net_net13, net_net14,

```

```

        net_net15, net_net16);
SUB6: entity Sub_full_adder_4bit port map (net_net13, net_net14,
        net_net15, net_net16, net_net9, net_net10, net_net11,
        net_net12, net_net4, netR2, net_net17, net_net18,
        net_net19, net_net20);
net_net21 <= netA3 and netB0;
net_net22 <= netA3 and netB1;
net_net23 <= netA3 and netB2;
net_net24 <= netA3 and netB3;
SUB7: entity Sub_full_adder_4bit port map (net_net17, net_net18,
        net_net19, net_net20, net_net21, net_net22,
        net_net23, net_net24, net_net4, netR3, netR4,
        netR5, netR6, netR7);
end architecture;

```

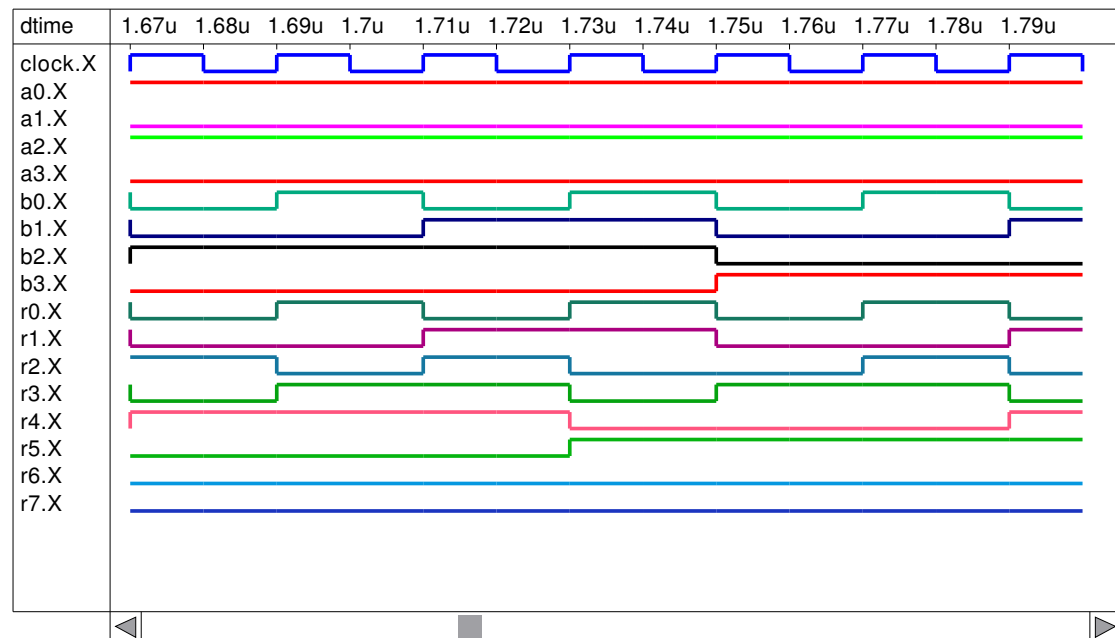


Figure 21: A section of the 4 bit by 4 bit combinational digital multiplier TimeList output waveforms.

Update number two: September 2006

Update number two in this tutorial series reports on the major changes that have taken place to Qucs digital simulation since the first update was posted on the Qucs

Web site roughly three months ago. During this period a number of significant, and very critical, extensions have been implemented. Previous releases concentrated on establishing a fundamental base for digital circuit simulation using the VHDL language. The primary vehicle for representing circuit signals being the VHDL bit and bit-vector signal types. The next release of Qucs (version 0.0.10) and FreeHDL (version 0.0.3) extends the allowed signal types to include IEEE `std_logic_1164` nine level logic, integers, and reals. Readers will appreciate that these changes are the result of a great deal of work by the Qucs team and must be considered as very much work in progress because not all the features offered by the FreeHDL implementation of the VHDL language are currently available via the Qucs schematic capture and VHDL text file simulation routes. Although a significant amount of testing has taken place it is likely that software bugs will come to light as more Qucs users try the new features - if you find a bug please report it by posting a note on the Qucs Web site. Adding new signal types to Qucs digital simulation affects all sections of the simulation route from schematic capture to plotting and tabulating input and output signals. Hence, although it may seem the wrong way round, the place to first implement the necessary changes to accommodate the new signal types is at the simulation results reporting stages of the Qucs package. In release 0.0.10 no attempt has been made to add the new signal types to the schematic capture part of the Qucs package.²¹ Recent work on the digital sections of the Qucs package has concentrated on (1) improvements to VHDL language entry using the Qucs colour coded VHDL text editor²², (2) modifications to FreeHDL which allow a cleaner interface between Qucs and FreeHDL, (3) upgrades to the data conversion of simulation results from the FreeHDL value change dump format to the native Qucs format, and (4) major changes to the results reporting routines that are accessed from the Qucs diagrams icon dialogue. A detailed list of the software changes and bug fixes can be found in the Qucs and FreeHDL change log files.

Simulating VHDL code using Qucs and FreeHDL.

The flow diagram drawn in Fig. 10 shows the relationship between Qucs and FreeHDL, and the sequence that takes place during digital circuit simulation. This flow diagram does not however, outline the details of the stages that are performed when converting (1) VHDL circuit code into a machine code simulation program, and (2) simulation output results into a format that can be plotted and tabulated by Qucs. These are illustrated in the flow diagram presented in Fig. 22. The shell script `qucsdigi` controls each of the stages in this sequence. A basic understanding

²¹Adding new signal types to Qucs schematic capture is on the to-do list.

²²A number of editor bugs have been fixed and it is now possible for users to define their own colour scheme for the various classes of VHDL reserved words and data types.

of the process employed by Qucs and FreeHDL is needed if users of the software are to be able to write meaningful VHDL code and simulate it using the two packages. VHDL code is either generated from a schematic diagram automatically by Qucs or entered using the Qucs VHDL text editor. The use of the schematic entry route was described in update one of these tutorial notes. However, a number of readers will probably have spotted that included in the VHDL code generated by Qucs are references to VHDL libraries. The VHDL language uses libraries to provide features that are not specified in the basic language definition but are commonly used by all language processing systems; two such libraries are STD and IEEE. When simulating digital circuits a basic knowledge of the structure of a simulation task and how these employ VHDL libraries is essential. This implies that users of the Qucs/FreeHDL software must appreciate how the system compiles and simulates a VHDL circuit simulation task. Once the VHDL simulation code has been entered via the VHDL text editor clicking the Qucs simulation button runs shell script `qucsdigi` performing the sequence shown in Fig. 22²³. Program `freehdl-v2cc` converts VHDL code into C++ functions. These are then compiled along with a main C++ function. The next stage in the sequence links the compiled object code with the object code from any references to items in the predefined VHDL libraries to produce an executable digital simulation program. This is then run by Qucs outputting a set of simulation results in value change dump (VCD) format²⁴. Finally a program called `qucsconv` converts the VCD simulation results into the Qucs native data format ready for post processing as graphical or tabular diagrams by Qucs.

²³For the FreeHDL package to operate correctly the directory where the software is installed must be included in the shell PATH from which Qucs is launched.

²⁴The value change dump language was originally designed as a simulation waveform interchange format for Verilog HDL. The specification of the VCD format can be found at <http://www-ee.eng.hawaii.edu/~msmith/ASICs/HTML/Verilog/LRM/HTML/15/ch15.2.htm>

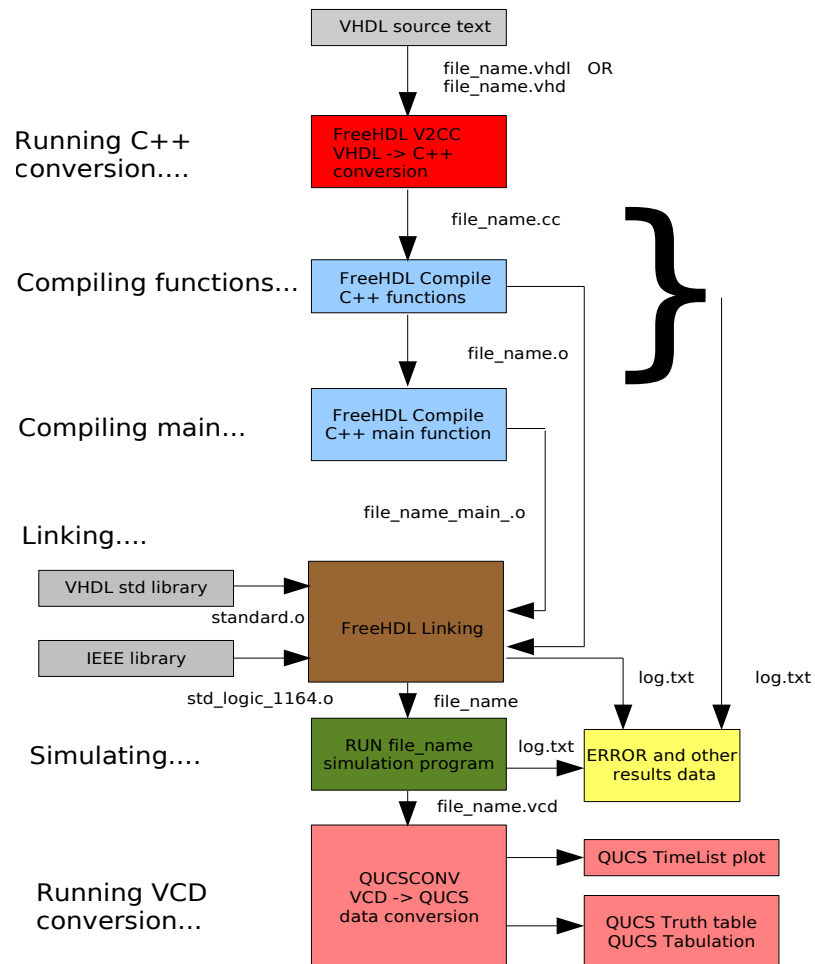


Figure 22: Detailed flow diagram showing VHDL code compilation and simulation results processing.

VHDL predefined packages and libraries.

All VHDL language processing systems provide a predefined VHDL package called `standard`. This package defines many of the fundamental VHDL data types, for example `bit`, `character`, `integer` and `real`. The predefined types, subtypes and other functions in the package `standard` are stored in a library called `STD`. The FreeHDL version of library `STD` includes an additional VHDL package called `textio` which is used to input and output signal data from and to files. A second library called `IEEE` defines (1) multivalued logic signals defined by nine different encoding values, making it possible to model digital circuits that are composed from different technology components, (2) logic signal subtypes and (3) an extensive range of useful functions, procedures and overloaded operators. The FreeHDL version of the `IEEE` library consists of the following packages:

1. `std_logic_1164`
2. `numeric_bit`
3. `math_real`
4. `numeric_std`
5. `std_logic_arith`
6. `std_logic_unsigned`
7. `vital_timing`

One other library is always defined by VHDL code processing systems namely the work library. This library holds user compiled VHDL entity/architecture design units.

VHDL simulation code structures.

In its most basic form VHDL circuit simulation code is structured as an entity-architecture test bench which includes input signal test information.²⁵ An example outline of the basic format is

```
entity testbench is
— entity body statements
end entity testbench;

—
architecture behavioural of testbench is
— architecture body statements
end architecture behavioural;
```

²⁵Test signals are often called test vectors.

VHDL data types, functions and operators in package standard are always visible to VHDL test bench code and reference to their use need not be added explicitly. However, if the test bench entity-architecture uses data types or other items defined in other libraries, for example the `std_logic` type in the IEEE library, then reference to them needs to be added before each entity-architecture pair where they are used. Libraries are referenced using the VHDL *library* and *use* statements. An example showing how these statements are employed is outlined in the following VHDL code segment:

```
library ieee;
use ieee.std_logic_1164.all;
—
entity testbench is
—  entity body statements
end entity testbench;
—
architecture behavioural of testbench is
—  architecture body statements
end architecture behavioural;
```

Here the VHDL code word *all* signifies that all items in a specific library are to be made available for use in the following entity/architecture pair; testbench in the above example. If more than one library is to be used then a library/use statement is needed for each library reference. Most complete VHDL circuit simulation programs consist of more than one entity/architecture pair. In such cases the circuit test bench, with its signal test vectors, must be the last entry in the program. An example of a more complex VHDL program structure is

```
library ieee;
use ieee.std_logic_1164.all;
—
entity compl is
—  entity body statements
end entity compl;
—
architecture behavioural of compl is
—  architecture body statements
end architecture behavioural;
—
library ieee;
use ieee.std_logic_1164.all;
—
entity comp2 is
—  entity body statements
```

```

end entity comp2;
—
architecture behavioural of comp2 is
—  architecture body statements
end architecture behavioural;

—
library ieee;
use ieee.std_logic_1164.all;
—
use work.all;
—
entity testbench is
—  entity body statements
end entity testbench;
—
architecture behavioural of testbench is
—  architecture body statements
end architecture behavioural;

```

During the conversion of VHDL code to a machine code simulation program each entity/architecture pair, prior to the final test bench entry, is compiled as a separate design unit and stored in the work library²⁶. Compiled design units held in the work library can be referenced in other entity/architecture models provided the VHDL statement *use work.all*;²⁷ is inserted in the VHDL simulation code prior to each entity/architecture statement where they are referenced.

²⁶The testbench entity/architecture pair is also, of course, compiled but this design unit is the one that is run as the executable simulation program.

²⁷References to individual items are also allowed by inserting, for example, *use.work.comb1*; *use.work.comb2*; in the VHDL code.

VHDL data types.

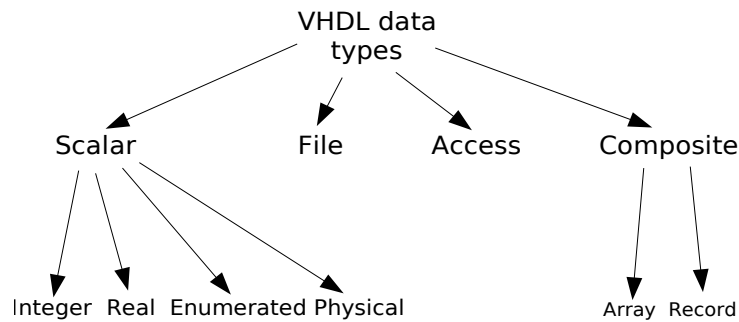


Figure 23: VHDL data types

The chart shown in Fig. 23 indicates the different data types that are available in the VHDL language. FreeHDL implements all these data types. In practical circuit simulation the different VHDL data types are normally used to specify (1) signals, (2) variables and (3) constants²⁸. During simulation Qucs/FreeHDL automatically stores the values of integer, real and enumerated bit signals as simulation time progresses. Furthermore, `bit_vector` and IEEE signal types including `std_logic_vector` are also stored. Signals of these types are then available for plotting and tabulation using the Timing, Truth table, Tabular and Cartesian output diagrams. Selected elements in user defined composite signals, those that are stored in arrays for example²⁹, can be assigned to the basic signal types then displayed.³⁰ An example of how this is done is given in later sections of these update tutorial notes. Note - the values of variables and constants are not recorded during simulation.

²⁸Type file is of course different in that it is used to store either test vectors, component data such as ROM contents and output simulation results.

²⁹Please note that signal types based on the composite type record will probably cause the Qucs simulation cycle to fail - work on this data type has been added to the to-do list.

³⁰Qucs/FreeHDL also automatically collects waveform data for composite signals based on arrays of bit and IEEE signal types. However, in the case of large arrays care is needed when plotting or tabulating these directly because the entire contents of an array is output each time a signal is displayed.

An example VHDL simulation employing integer signals.

The following VHDL code demonstrates how the integer data type can be used to represent signals. In this example signals A, B change state on the rising edge of clock clk. The code tests the addition of integer signals and constants using arithmetic operators defined in library STD.³¹ The results from this simulation are shown in Fig. 24.

— *A very basic test of data type integer.*

```

entity testbench is
end entity testbench;
—
architecture behavioural of testbench is
  signal A, B, C : integer := 0;
  signal clk : bit;
  begin
  p0 : process is — Generate clock signal.
    begin
      clk <= '0';   wait for 10 ns;
      clk <= '1';   wait for 10 ns;
    end process p0;
  —
  p1 : process (clk) is
    begin
      if (clk'event and clk='1') then
        A <= A + 1;
        B <= B + 2;
      end if;
    end process p1;
    C <= A + B ;
  end architecture behavioural;

```

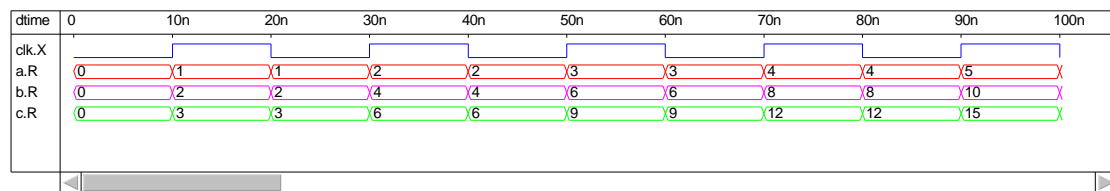


Figure 24: Output results for a simple test bench example employing integer signals.

³¹The specification for the FreeHDL library STD can be found in text file freehdl-0.0.3/std/standard.vhdl.

Multivalued logic.

Although signal types `bit` and `bit_vector` are widely employed when simulating digital systems one of their great weaknesses is the fact that it is difficult to represent signal bus systems simply using only logic '0' and logic '1' signal encoding. Moreover, circuits where bus signal contention occurs often result in simulation failure. The IEEE `std_logic_1164` package overcomes this limitation through the introduction of a multivalued logic system which defines nine different logic values to represent signal types and signal strengths. Not only is the bus contention problem solved through logic resolving functions but the multivalued logic system allows devices constructed from different manufacturing technologies to be simulated at the same time, ensuring that the simulation process mirrors real circuit design practices. The next two simulation examples introduce the nine value logic system and demonstrate its use in the design of digital bus systems. Signals of type `real` are also introduced to show their representation by Qucs. Listed below is the VHDL code for a basic simulation which generates a set of IEEE `std_logic`, integer and real signals. Figure 25 illustrates how the Qucs Timing diagram displays different signal types. A section of tabulated results are also given in Fig. 26.

```
library ieee;
use ieee.std_logic_1164.all;
--
entity testbench is
end entity testbench;
--
architecture behavioural of testbench is
signal clk : bit;
signal bv1 : bit_vector(8 downto 0);
signal stdl1 : std_logic_vector(8 downto 0);
signal INT1 : integer := 0;
signal INT2 : integer := 99;
signal R1 : real := 0.33;
signal R2 : real := 99.0;
signal R3 : real := 0.0;
signal R4 : real := 0.0;
begin
p0 : process is
begin
    clk <= '0'; wait for 10 ns;
    clk <= '1'; wait for 10 ns;
end process p0;
--
```

```

p1 : process (clk) is
    variable v1 : integer := 0;
    begin
        if (clk'event and clk = '1') then
            v1 := v1+1;
            case v1 is
                when 1 => bv1 <= "000000000"; stdl1 <= "000000000";
                when 2 => bv1 <= "000000001"; stdl1 <= "000000001";
                when 3 => bv1 <= "000000011"; stdl1 <= "00000001X";
                when 4 => bv1 <= "000000111"; stdl1 <= "0000001XZ";
                when 5 => bv1 <= "000001111"; stdl1 <= "000001XZU";
                when 6 => bv1 <= "000011111"; stdl1 <= "00001XZUW";
                when 7 => bv1 <= "000111111"; stdl1 <= "0001XZUWL";
                when 8 => bv1 <= "001111111"; stdl1 <= "001XZUWLH";
                when 9 => bv1 <= "111111111"; stdl1 <= "01XZUWLH";
                when others => v1 := 0;
            end case;
        end if;
    end process p1;
p3 : process (clk) is
    begin
        if (clk'event and clk='1') then
            INT1 <= INT1 + 1;
            INT2 <= INT2 -20;
        end if;
    --
        if (INT1 >= 9) then
            INT1 <= 0;
            INT2 <= 99;
        end if;
    end process p3;
--
p4 : process (clk) is
    Variable V2 : real;
    begin
        if (clk'event and clk='1') then
            R1 <= R1 + 1.0;
            R2 <= R2 -20.0;
            R3 <= R1*R2;
            R4 <= R2/(R1+0.0001);
        end if;
    --
        if (R1 >= 20.0) then

```

```

        R1 <= 0.0;
        R2 <= 99.0;
    end if;
end process p4;
end architecture behavioural;

```

 


Figure 25: Output results illustrating the TimeList representation of signals.

The VCD waveform interchange standard encodes digital signals as four different logic levels. These are '0', '1', 'Z' (high impedance) and 'X' (unknown). Table 7 lists how the nine `ieee.std_logic` signal levels are represented using the VCD format. Until the VCD standard is revised the Qucs/FreeHDL package is restricted to displaying simulation output data using the basic '0', '1', 'Z' and 'X' signal encoding. The next example shows how the IEEE `std_logic` signal type can be used to simulate bus logic. The demonstration has been kept simple in order to keep the VHDL code short. The code fragment simulates two tri-state buffers which

VHDL signal levels	VCD
'0' Forcing logic 0	'0'
'1' Forcing logic 1	'1'
'X' Forcing unknown	'X'
'Z' High impedance	'Z'
'U' Uninitialised	'X'
'W' Weak unknown	'0'
'L' Weak logic 0	'0'
'H' Weak logic 1	'1'
'-' Don't care	'X'

Table 7: IEEE multivalue logic and VCD representation.

pass their outputs to bus drivers who's outputs connect on a common signal bus. The bus drivers ensure that the outputs from the tri-state buffers are kept separate before combining onto the common bus line. This allows the output signals from the tri-state buffers and the combined signal to be plotted separately. The resulting waveforms clearly show the `std_logic` resolution function in operation, see Fig. 27 . Note the effect of the 7 ns delay on the plotted waveforms and the use of the VHDL generic statement to set the invert device delay value.

— *Demonstration of a simple bus structure using*
— *the IEEE std_logic data type.*

```

library ieee;
use ieee.std_logic_1164.all;
—
entity buf is
    generic(delay : time := 0 ns);
    port (in1, control : in std_logic;
        out1 : out std_logic
        );
end entity buf;
architecture behavioural of buf is
begin
p0 : process (in1, control) is
    begin
        if (control = '1') then out1 <= in1 after delay;
        else out1 <= 'Z';
        end if;
    end process p0;
end architecture behavioural;

```

```

—
library ieee;
use ieee.std_logic_1164.all;
—
entity invert is
    generic(delay : time := 0 ns);
    port (in1 : in std_logic;
          out1 : out std_logic
          );
end entity invert;
—
architecture behavioural of invert is
begin
    out1 <= not in1 after delay;
end architecture behavioural;
—
library ieee;
use ieee.std_logic_1164.all;
—

entity buf2 is
    port (in1 : in std_logic;
          out1 : out std_logic
          );
end entity buf2;
—
architecture dataflow of buf2 is
begin
    out1 <= in1;
end architecture dataflow;
—
library ieee;
use ieee.std_logic_1164.all;
—
use work.all;
—
entity testbench is
end entity testbench;
—
architecture structural of testbench is
signal data_in_1, data_in_2 : std_logic;
signal data_out_1, data_out_2 : std_logic;
signal data_control, control_buf1 : std_logic;

```

```

signal result : std_logic;
—
begin
p0 : process is
    begin
        data_in_1 <= '0'; wait for 5 ns;
        data_in_1 <= '1'; wait for 5 ns;
    end process p0;
—
    data_in_2 <= not data_in_1;
—
p1 : process is
    begin
        data_control <= '1'; wait for 40 ns;
        data_control <= '0'; wait for 40 ns;
    end process p1;
—
clg1 : entity buf      port map(in1 => data_in_1, control => data_control,
                                out1 => data_out_1);
clg2 : entity invert  generic map (delay => 7 ns)
                                port map(in1 => data_control, out1 => control_buf1);
clg3 : entity buf      port map(in1 => data_in_2, control => control_buf1,
                                out1 => data_out_2);
clg4 : entity  buf2    port map(in1 => data_out_1, out1 => result);
clg5 : entity  buf2    port map(in1 => data_out_2, out1 => result);
—
end architecture structural;

```

▲	dtime	clk.X	int1.R	int2.R	r1.R	r2.R	r3.R	r4.R	bv1.X	stdl1.X
	0	0	0	99	0.33	99	0	0	00000000	XXXXXXXXXX
	1e-8	1	1	79	1.33	79	32.7	300	00000000	00000000
	2e-8	0	1	79	1.33	79	32.7	300	00000000	00000000
	3e-8	1	2	59	2.33	59	105	59.4	00000001	00000001
	4e-8	0	2	59	2.33	59	105	59.4	00000001	00000001
	5e-8	1	3	39	3.33	39	137	25.3	00000011	0000001X
	6e-8	0	3	39	3.33	39	137	25.3	00000011	0000001X
	7e-8	1	4	19	4.33	19	130	11.7	00000111	000001XZ
	8e-8	0	4	19	4.33	19	130	11.7	00000111	000001XZ
	9e-8	1	5	-1	5.33	-1	82.3	4.39	00001111	00001XZX
	1e-7	0	5	-1	5.33	-1	82.3	4.39	00001111	00001XZX
	1.1e-7	1	6	-21	6.33	-21	-5.33	-0.188	00001111	00001XZX0
	1.2e-7	0	6	-21	6.33	-21	-5.33	-0.188	00001111	00001XZX0
	1.3e-7	1	7	-41	7.33	-41	-133	-3.32	00011111	0001XZX00
	1.4e-7	0	7	-41	7.33	-41	-133	-3.32	00011111	0001XZX00
	1.5e-7	1	8	-61	8.33	-61	-301	-5.59	00111111	001XZX001
	1.6e-7	0	8	-61	8.33	-61	-301	-5.59	00111111	001XZX001
	1.7e-7	1	9	-81	9.33	-81	-508	-7.32	11111111	01XZX001X
	1.8e-7	0	0	99	9.33	-81	-508	-7.32	11111111	01XZX001X
▼	1.9e-7	1	1	79	10.3	-101	-756	-8.68	11111111	01XZX001X

	clk.X	int1.R	int2.R	r1.R	r2.R	r3.R	r4.R	bv1.X	stdl1.X
00000	0	0	99	0.33	99	0	0	000000000	XXXXXXXXXX
00001	1	1	79	1.33	79	32.67	299.909	000000000	000000000
00010	0	1	79	1.33	79	32.67	299.909	000000000	000000000
00011	1	2	59	2.33	59	105.07	59.394	000000001	000000001
00100	0	2	59	2.33	59	105.07	59.394	000000001	000000001
00101	1	3	39	3.33	39	137.47	25.3208	000000011	00000001X
00110	0	3	39	3.33	39	137.47	25.3208	000000011	00000001X
00111	1	4	19	4.33	19	129.87	11.7114	000000111	0000001XZ
01000	0	4	19	4.33	19	129.87	11.7114	000000111	0000001XZ
01001	1	5	1	5.33	1	82.27	4.38789	000001111	000001XZX
01010	0	5	1	5.33	1	82.27	4.38789	000001111	000001XZX
01011	1	6	21	6.33	21	5.33	0.187614	000011111	00001XZX0
01100	0	6	21	6.33	21	5.33	0.187614	000011111	00001XZX0
01101	1	7	41	7.33	41	132.93	3.31748	000111111	0001XZX00
01110	0	7	41	7.33	41	132.93	3.31748	000111111	0001XZX00
01111	1	8	61	8.33	61	300.53	5.59338	001111111	001XZX001
10000	0	8	61	8.33	61	300.53	5.59338	001111111	001XZX001
10001	1	9	81	9.33	81	508.13	7.32284	111111111	01XZX001X
10010	0	0	99	9.33	81	508.13	7.32284	111111111	01XZX001X
10011	1	1	79	10.33	101	755.73	8.68158	111111111	01XZX001X
10100	0	1	79	10.33	101	755.73	8.68158	111111111	01XZX001X

Figure 26: Output results illustrating tabular representation of signals.

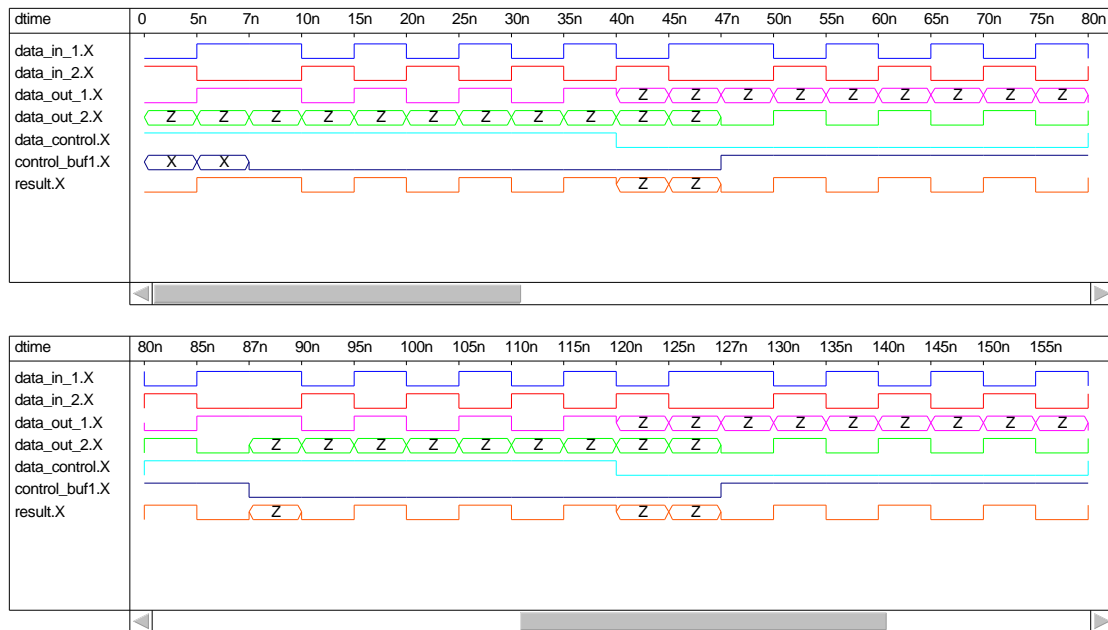


Figure 27: Signal waveforms for the simple bus example.

Run debugging of VHDL simulation code.

The VHDL language has a number of built in features that allow the debugging of VHDL code at simulation time. In this section the VHDL reserved words *assert*, *report* and *severity* are introduced and their use as code debugging aids explained by way of a more detailed design example. In the previous digital tutorial update a structural design of a 4 bit digital multiplier was introduced as an example that employed the Qucs schematic capture digital simulation route. The next example extends the previous multiplier design to 16 bits. However, at a structural level the larger multiplier becomes very detailed and it's design can be prone to error. To demonstrate the power of VHDL the 16 bit multiplier has been redesigned at a functional level. A block diagram of the multiplier simulation test bench is given in Fig. 28: firstly a clock strobes a data generator unit which generates a sequence of integer numbers. These are converted to 16 `bit_vectors` and applied to the 16 bit multiplier unit as inputs `x` and `y`; secondly the 16-bit multiplier on sensing a change in inputs `x` or `y` converts these signals from 16 `bit_vectors` to integers, multiplies them and finally converts the integer result to 32 `bit_vector` output `Res_bit`. Although standard library STD defines arithmetic operations for integers it does not provide functions for the conversion of integers to `bit_vectors` or the reverse operation. The following VHDL listing gives the complete simulation test bench

program for the 16 bit multiplier including the required data conversion functions. VHDL debug or message reporting code using the reserved words `assert`, `report` and `severity` have been added to the `data_generator` and `functional_multiplier` architecture code. During simulation these text strings, and the simulation time when they were actioned, are written to the Qucs log.txt file, giving a trace record of the simulation activity. In cases where an error occurs at severity level failure the simulation will terminate. FreeHDL allows VHDL report statements without an accompanying `assert` statement.³² A typical Timing diagram plot for this design is shown in Fig. 29

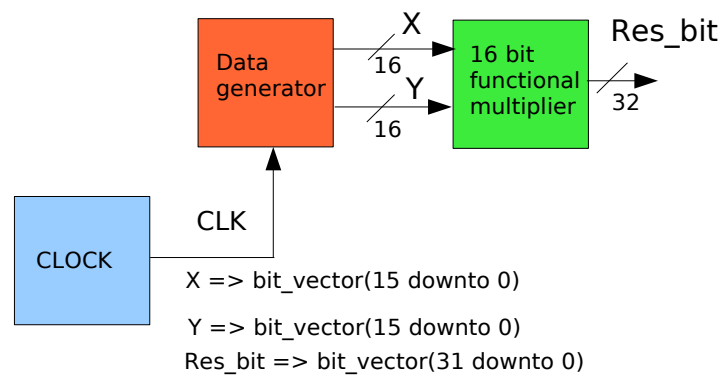


Figure 28: Block diagram of a 16 bit functional multiplier.

— *16 bit digital multiplier example.*
— *Simulation trace using assert, report and severity statements.*
—

```

entity clock is
    port( clk : out bit);
end entity clock;
—
architecture behavioural of clock is
begin
p0 : process is

```

³²One of the changes at the 1993 revision of the IEEE VHDL 1076-1987 standard was to allow report statements without the previous mandatory `assert` clause. FreeHDL attempts to comply with the 1993 revision.

```

        begin
            clk <= '0' ; wait for 10 ns;
            clk <= '1' ; wait for 10 ns;
        end process p0;
end architecture behavioural;
--
entity data_generator is
    port( clk : in bit;
          x, y : out bit_vector(15 downto 0)
        );
end entity data_generator;
--
architecture behavioural of data_generator is
type mem_array_16 is array(1 to 8) of integer;
signal count : integer := 0;
--
function integer_to_vector_16(int_no : integer) return bit_vector
is
variable ni : integer;
variable return_value : bit_vector(15 downto 0);
begin
    assert (ni < 0)
        report "Function_integer_to_vector_32:_integer_number_must_be_>=0"
        severity failure;
    ni := int_no;
    for i in return_value'Reverse_Range loop
        if ( (ni mod 2) = 1 ) then return_value(i) := '1';
        else return_value(i) := '0';
        end if ;
        ni := ni/2;
    end loop;
    return return_value;
end integer_to_vector_16;
--
begin
p1 : process(clk) is
    variable xi : mem_array_16 := (1, 2, 3, 4, 5, 6, 7, 8);
    variable yi : mem_array_16 := (2, 4, 6, 8, 10, 12, 14, 16);
    variable xh, yh : integer;
    variable counti : integer;
begin
        counti := count+1;

```

```

        if (counti > 8 ) then
            counti := 1;
        end if;
        xh := xi(counti);
        yh := yi(counti);
        x <= integer_to_vector_16(xh);
        y <= integer_to_vector_16(yh);
        count <= counti;
        report "In_process_p1.data_generator.";
    end process p1;
end architecture behavioural;
--
--
entity functional_multiplier is
    port( x, y : in bit_vector(15 downto 0);
          res_bit : out bit_vector(31 downto 0)
    );
end entity functional_multiplier;
--
--
architecture behavioural of functional_multiplier is
--
function vector_to_integer(v1 : bit_vector) return integer is
    variable return_value : integer :=0;
    alias v2 : bit_vector(v1'length-1 downto 0) is v1;
begin
    for i in v2'high downto 1 loop
        if (v2(i) = '1') then
            return_value := (return_value+1)*2;
        else
            return_value := return_value*2;
        end if;
    end loop;
    if v2(0) = '1' then return_value:= return_value+1;
    end if;
    return return_value;
end vector_to_integer;
--
function integer_to_vector_32(int_no : integer) return bit_vector
is
    variable ni : integer;
    variable value : bit_vector(31 downto 0);
begin

```



```

    assert (ni < 0)
        report "Function_integer_to_vector_32:_integer_number_must_be_>=0"
        severity failure;
    ni := int_no;
    for i in 0 to 31 loop
        if ( (ni mod 2) = 1 ) then value(i) := '1';
        else value(i) := '0';
        end if ;
        if ni > 0 then ni := ni/2;
        else ni := (ni-1)/2;
        end if;
    end loop;
    return value;
end integer_to_vector_32;
--
begin
p0 : process (x,y) is
    variable xi, yi, prod_mult : integer;
    begin
        xi := vector_to_integer(x);
        yi := vector_to_integer(y);
        prod_mult := xi*yi;
        res_bit <= integer_to_vector_32(prod_mult);
        report "In_process_p1.functional_multiplier";
    end process p0;
end architecture behavioural;
--
entity test2_vhdl_1 is
end entity test2_vhdl_1;
--
architecture behavioural of test2_vhdl_1 is
    signal clk : bit;
    signal x, y : bit_vector(15 downto 0);
    signal res_bit : bit_vector(31 downto 0);
--
begin
d1 : entity work.clock port map (clk);
d2 : entity work.data_generator port map(clk, x, y);
d3 : entity work.functional_multiplier port map ( x, y, res_bit);

end architecture behavioural;

```

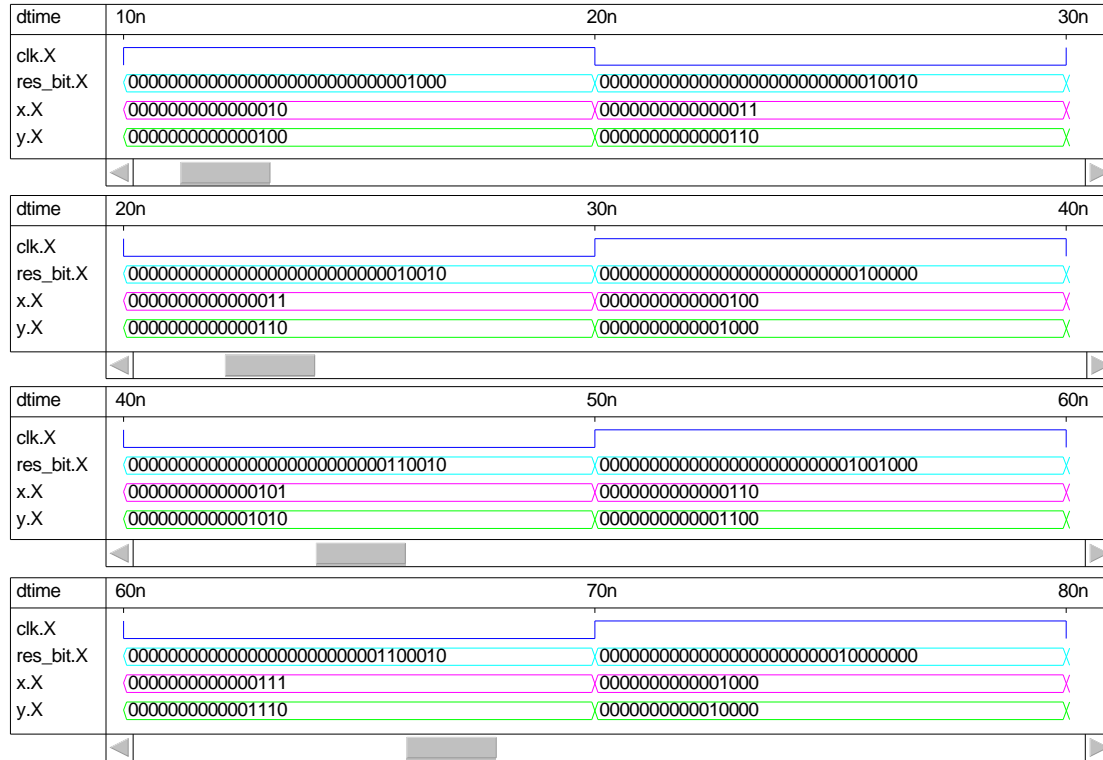


Figure 29: Typical timing diagram for the 16 bit functional multiplier.

More advanced output debug messages, and results tables, can be written to Qucs message file log.txt by using the predefined data handling routines in STD library package textio³³. This package contains functions for reading and writing STD data types from and to files³⁴. The next segment of VHDL code illustrates how a simple table of results can be written to file log.txt. The results table is shown in Table 8.

— *Test textio package.*

```
library STD;
use STD.textio.all;

entity Qucs_write_test is
```

³³The specification for the FreeHDL package textio can be found in text file freehdl-0.0.3/std/textio.vhdl.

³⁴VHDL allows data to be read from and written to the standard input and output streams as well as user defined files. At this time only writing data to file log.txt and reading data from user defined data files has been tested. Please note that the use of the textio package is very much a cutting edge feature of the Qucs/FreeHDL software and is probably not bug free.

```

end entity Qucs_write_test;
--
architecture behavioural of Qucs_write_test is
begin
write_test: process is
    variable input_line, output_line : line;
    variable int1 : integer := 10;
begin
    write(output_line, string'(" ") );
    writeline(output, output_line);
    write(output_line, string'("String->log.txt" ) );
    writeline(output, output_line);
--
test_L1 :    for ic in 1 to 5 loop
                int1 := int1 + 1;
                write(output_line, string'("int1=" ) );
                write(output_line, int1);
                write(output_line, string'("int1^2=" ) );
            );

                write(output_line, int1*int1);
                writeline(output, output_line);
            end loop test_L1;
            report "Finished_test_for_loop.";
        end process write_test;
end architecture behavioural;

```

```

Output:
-----
Starting new simulation on Thu 24. Aug 2006 at 13:10:56
running C++ conversion... done.
compiling functions... done.
compiling main... done.
linking... done.
simulating...
Output to STD output -> log.txt
int1 = 11    int1^2 = 121
int1 = 12    int1^2 = 144
int1 = 13    int1^2 = 169
int1 = 14    int1^2 = 196
int1 = 15    int1^2 = 225
0 fs + 0d: NOTE: Finished test for loop.
running VCD conversion... done.
Simulation ended on Thu 24. Aug 2006 at 13:10:57
Ready.
Errors:
-----

```

Table 8: Log.txt file showing tabular output results.

Testing digital systems using test vectors stored on disk.

In an attempt on my part to review all the new features introduced in the previous sections of this update the final example demonstrates how test vectors stored on disk, as a text file, can be read by the simulation program at the start of a simulation, then applied to the inputs of the digital system under test. The code for this example is given in the following listing:

```
— Testing digital circuits using test vectors  
— stored as a text file on disk.  
—
```

```
entity comb1 is  
    port (a, b, c, d : in bit;  
          y : out bit  
          );  
end entity comb1;
```

```
—  
architecture dataflow of comb1 is  
begin  
    y <= (a nand b) or (c and d);  
end architecture dataflow;
```

```
—  
library STD;  
use STD.textio.all;
```

```
—  
entity testbench is  
end entity testbench;
```

```
—  
architecture behavioural of testbench is  
signal clock : bit;  
signal v1, v2, v3, v4, y_out : bit;  
type array_list is array (1 to 20) of bit;  
signal v1sd, v2sd, v3sd, v4sd : array_list;
```

```
—  
Procedure store_data (variable number : out integer) is  
    variable d1, d2, d3, d4 : bit;  
    variable in_line, out_line : line;  
    variable i : integer ;  
    variable my_string : string(1 to 20) := cr & "Constrained_string" & cr;  
    file infile : text open read_mode is "/mnt/hda2/qucs-0.0.10f/test1_data";  
begin  
    report my_string;  
    i := 1;  
    while not ( endfile(infile) ) loop
```

```

    readline(infile , in_line);
    read(in_line , d4);
    read(in_line , d3);
    read(in_line , d2);
    read(in_line , d1);
    v1sd(i) <= d1;
    v2sd(i) <= d2;
    v3sd(i) <= d3;
    v4sd(i) <= d4;
    report "In_file_read_loop.";
    i := i+1;
    if (i > 20) then exit;
    end if;
    number:= i;
end loop;
end procedure store_data;
—
begin
p0 : process is — Generate a clock signal.
    begin
        clock <= '1'; wait for 10 ns;
        clock <= '0'; wait for 10 ns;
    end process p0;
—
g0 : entity work.comb1 port map (v1, v2, v3, v4, y_out);
—
p1 : process is — Read test vectors from disk and
    apply data to circuit inputs.
    variable no_reads : integer;
    variable in_line , out_line : line;
begin
    store_data(no_reads);
    write(out_line , string'("count_====") );
    write(out_line , no_reads-1);
    writeline(output , out_line);
—
    for k in 1 to no_reads-1 loop — Count up.
        wait until (clock'event and clock='1');
        v1 <= v1sd(k);
        v2 <= v2sd(k);
        v3 <= v3sd(k);
        v4 <= v4sd(k);
        write(out_line , string'("Time_="),left , 8 );

```

```

        write(out_line , now, right , 10);
        write(out_line , string'("_Test_vectors_>_"),right , 20 );
        write(out_line , v4, left , 2 );
        write(out_line , v3, left , 2 );
        write(out_line , v2, left , 2);
        write(out_line , v1, left , 2);
        write(out_line , string'("k=_"), right , 10 );
        write(out_line ,k);
        writeline(output,out_line);
        wait until (clock'event and clock='0');
    end loop;
--
    for k in  no_reads-1 downto 1 loop -- Count down.
        wait until (clock'event and clock='1');
        v1 <= v1sd(k);
        v2 <= v2sd(k);
        v3 <= v3sd(k);
        v4 <= v4sd(k);
        write(out_line , string'("Time=_"),left , 8 );
        write(out_line , now, right , 10);
        write(out_line , string'("_Test_vectors_>_"),right , 20 );
        write(out_line , v4, left , 2 );
        write(out_line , v3, left , 2 );
        write(out_line , v2, left , 2);
        write(out_line , v1, left , 2);
        write(out_line , string'("k=_"), right , 10 );
        write(out_line ,k);
        writeline(output,out_line);
        wait until (clock'event and clock='0');
    end loop;
    wait;
end process p1;
end architecture behavioural;

```

Although the listing above is relatively short, careful study of it's contents should allow readers to identify many of the new Qucs/FreeHDL features introduced earlier. Moreover in some sections, the code illustrates extra features which will be familiar to those Qucs/FreeHDL users who have a more advanced knowledge of the VHDL language. These are listed below with a number of general points:

- The VHDL code simulates the performance of a simple combinational logic circuit called comb1: this has four inputs (a, b, c, d) of type bit and one output (y) of type bit³⁵.

³⁵Type bit was chosen for this example rather than one of the IEEE signal types because

- The testbench being simulated consists of two processes: process p0 generates a clock signal with a period of 20 ns; process p1 inputs test data held in file `test1_data`³⁶ and stores it in four signal arrays (v1sd, v2sd, v3sd and v4sd), applying this data to the inputs of the circuit under test at the leading edges of the clock pulse. Note process p1 only executes once due to the wait statement at its end.
- An instantiation of the `comb1` component is included in the testbench architecture. Note the use of the VHDL *entity work.comb1* construction, this is an alternative for *use work.all*;
- The test vector data held in file `test_data` is read by procedure `store_data` which returns the number of lines of data read in variable `number`. File handling, including reading data from disk, is undertaken with predefined routines in package `textio`.
- The first *report* statement in procedure `store_data` writes string `my_string` to file `log.txt`. `My_string` is an example of the VHDL constrained string type, consisting of non-printable control characters³⁷ concatenated with printable characters.
- Two loops are employed in process p1 to apply signal test vectors to the input of `comb1`: the first loop counts up from one and the second loop counts down from the number of lines of test vectors read by procedure `store_data`, effectively generating test vectors in a way similar to using an up-down pattern generator counter. Note that the signal data is applied to the circuit under test on the rising edge of the clock signal and that the applied signal vector sequence is really up to the imagination of the VHDL programmer.
- The write statements in the process p1 for loops demonstrate the formatted version of the `textio` write statement. This greatly assists in setting up tables of results. Table 9 gives a typical `log.txt` content for the `comb1` test simulation.
- In process p1 signals v1, v2, v3 and v4 are assigned an indexed value from (type `array_list`) v1sd, v2sd, v3sd and v4sd signals. During simulation

package `textio` does not handle the IEEE multivalued logic types.

³⁶I use the Knoppix version of the Linux/GNU operating system for all work on the Qucs project. The absolute location of the test data file will depend on where Qucs and FreeHDL have been installed and the location where work files are kept.

³⁷Type character in package standard lists the two letter codes used by VHDL to represent non-printable control characters.

Qucs/FreeHDL stores signal values as a simulation progresses. Hence, it is theoretically possible to display both the standard and composite signal types. A typical waveform plot for signals `v1`, `v2`, `v3`, `v4` and `y_out` is given in Fig. 30. Fig. 31 illustrates a waveform plot of the composite signals `v1sd`, `v2sd`, `v3sd` and `v4sd`. In Fig. 31 each group is plotted at a clock edge change yielding identical groups of values; each vertical set of bits represents the bit values for a single line in file `test1_data`. Compare the displayed values in Fig. 31 with the contents of the `test1_data` file shown in Fig. 32. As mentioned before some care is needed when plotting, or tabulating, composite signals, particularly when the array sizes are large; array dimensions above roughly 50 become difficult to plot on a normal resolution screen. In such cases it is better to slice part of an array and assign the required values to a signal that can be easily displayed.

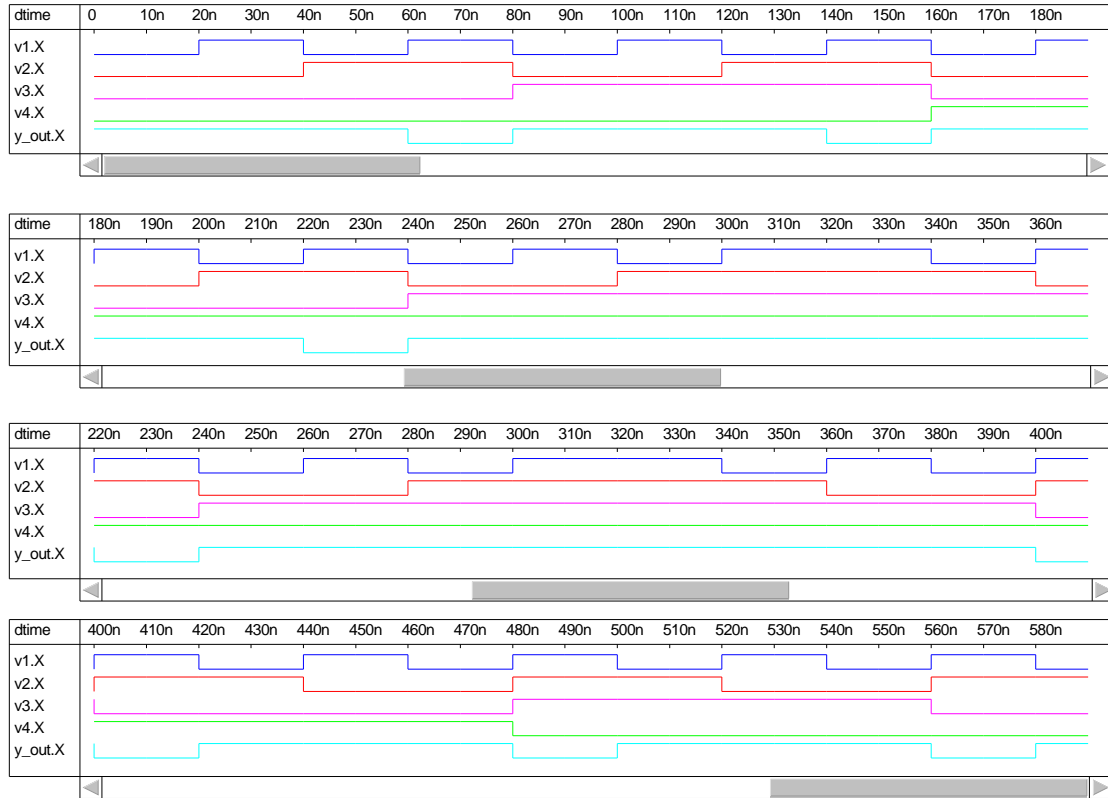


Figure 30: Typical timing diagram for comb1 simulation.

Output:

```

Starting new simulation on Fri 25. Aug 2006 at 14:35:48
running C++ conversion... done.
compiling functions... done.
compiling main... done.
linking... done.
simulating...
0 fs + 0d: NOTE:
Constrained string
0 fs + 0d: NOTE: In file read loop.
.
0 fs + 0d: NOTE: In file read loop.
count =      16
Time =         0 ns    Test vectors ->  0 0 0 0          k = 1
Time =        20 ns    Test vectors ->  0 0 0 0          k = 2
Time =        40 ns    Test vectors ->  0 0 0 1          k = 3
Time =        60 ns    Test vectors ->  0 0 1 0          k = 4
.
Time =       200 ns    Test vectors ->  1 0 0 1          k = 11
Time =       220 ns    Test vectors ->  1 0 1 0          k = 12
Time =       240 ns    Test vectors ->  1 0 1 1          k = 13
Time =       260 ns    Test vectors ->  1 1 0 0          k = 14
Time =       280 ns    Test vectors ->  1 1 0 1          k = 15
Time =       300 ns    Test vectors ->  1 1 1 0          k = 16
Time =       320 ns    Test vectors ->  1 1 1 1          k = 16
Time =       340 ns    Test vectors ->  1 1 1 1          k = 15
Time =       360 ns    Test vectors ->  1 1 1 0          k = 14
Time =       380 ns    Test vectors ->  1 1 0 1          k = 13
Time =       400 ns    Test vectors ->  1 1 0 0          k = 12
.
Time =       560 ns    Test vectors ->  0 1 0 0          k = 4
Time =       580 ns    Test vectors ->  0 0 1 1          k = 3
running VCD conversion... done.
Simulation ended on Fri 25. Aug 2006 at 14:35:50
Ready.
Errors:

```

Table 9: An edited version of the formatted tabular output results written to file log.txt.

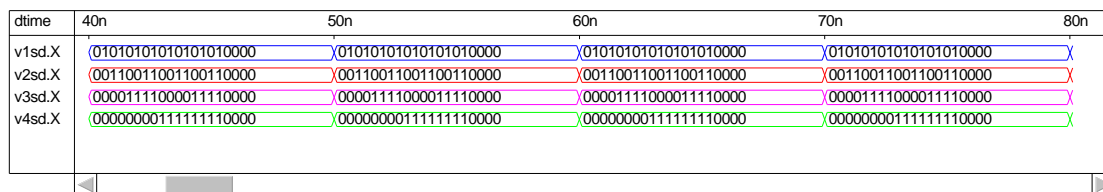


Figure 31: Typical timing diagram for composite signals v1sd, v2sd, v3sd and v4sd.

```

0 0 0 0
0 0 0 1
0 0 1 0
0 0 1 1
0 1 0 0
0 1 0 1
0 1 1 0
0 1 1 1
1 0 0 0
1 0 0 1
1 0 1 0
1 0 1 1
1 1 0 0
1 1 0 1
1 1 1 0
1 1 1 1

```

Figure 32: Comb1 simulation test vectors.

End note

Qucs 0.0.8 added digital simulation to the impressive list of features already available in the Qucs package. The 0.0.8 release represented a significant step forward in the development of the Qucs project. The fact that there were bugs in the first version of the digital simulator was not surprising given the complexity of the software. Release 0.0.9 goes a long way to correcting the most annoying of these bugs. It also adds a number of new features, the most notable being the new VHDL editor and the automatic generation of component symbols from hand crafted VHDL

model code. Qucs 0.0.10 and FreeHDL 0.0.3 adds a range of new features to the software, particularly important are the use of the IEEE `std_logic_1164` package and the file handling routines found in the `textio` package. My thanks to Michael Margraf and Stefan Jahn for all their encouragement during the period that I have been testing the Qucs VHDL digital simulation and the subsequent writing of these notes.